

---



# Optoelectronics Lab


Basic Concepts

# Charge & Current

- Charge is the quantity of electricity responsible for electric phenomena.
- Current is the time rate of flow of electric charge past a given point. The unit of current is the ampere (A); an ampere is 1 coulomb per second.

$$i = \frac{dq}{dt}$$

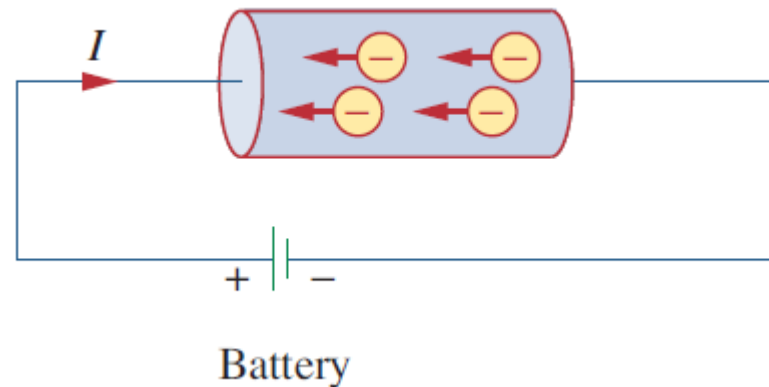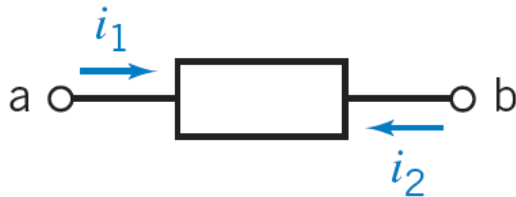

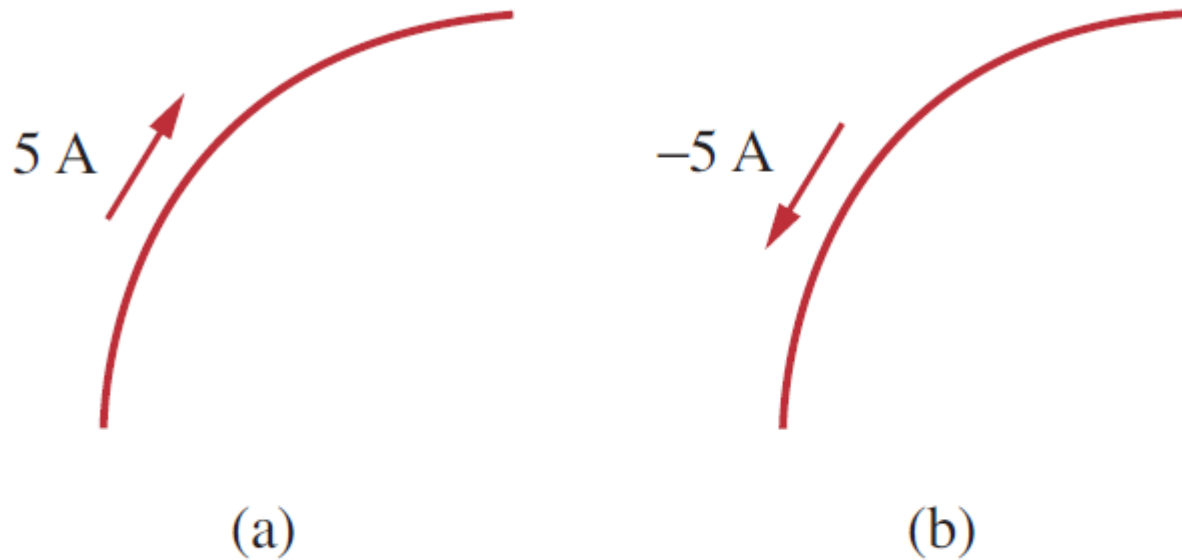

**Figure 1.5**

Conventional current flow: (a) positive current flow, (b) negative current flow.

# Voltage

---


- The voltage across an element is the work (energy) required to move a unit positive charge from the – (negative) terminal to the + (positive) terminal. The unit of voltage is the volt, V.


$$v_{ab} \triangleq \frac{dw}{dq}$$

1 volt = 1 joule/coulomb = 1 newton-meter/coulomb

# Polarity of Voltage

---

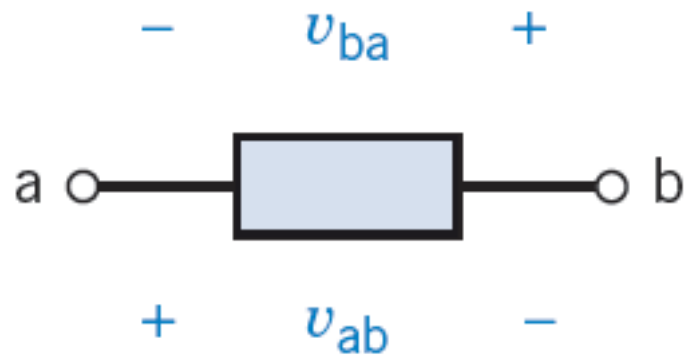

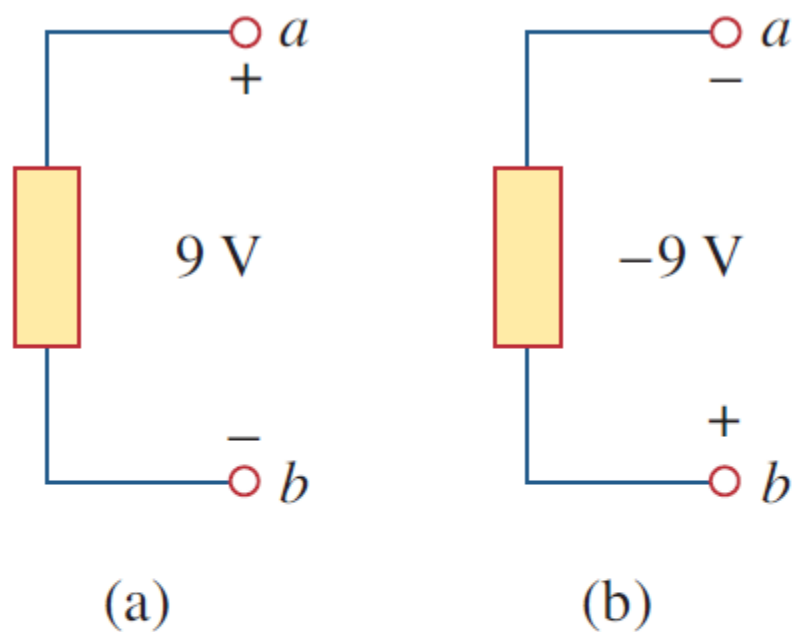


### Figure 1.7

Two equivalent representations of the same voltage  $v_{ab}$ : (a) Point  $a$  is 9 V above point  $b$ ; (b) point  $b$  is  $-9$  V above point  $a$ .


# Resistors

- Ohm's Law

$$v = Ri$$

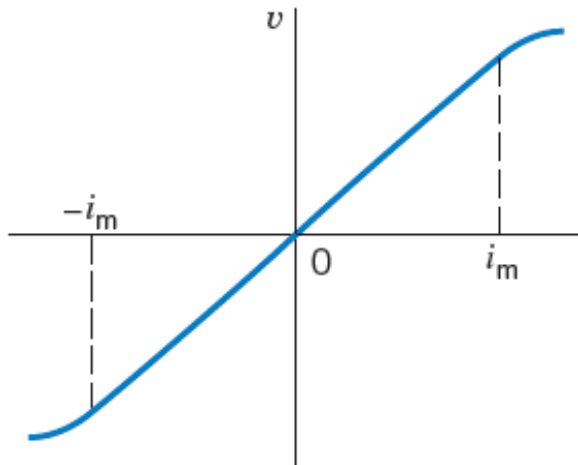

**FIGURE 2.4-3** A resistor operating within its specified current range,  $\pm i_m$ , can be modeled by Ohm's law.

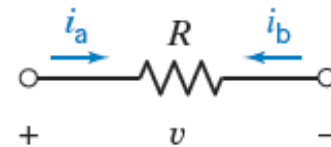

**FIGURE 2.4-4** A resistor with element current and element voltage.


$$i_a = -i_b$$

$$v = Ri_a$$


$$v = -Ri_b$$

# Short Circuit/Open Circuit

---

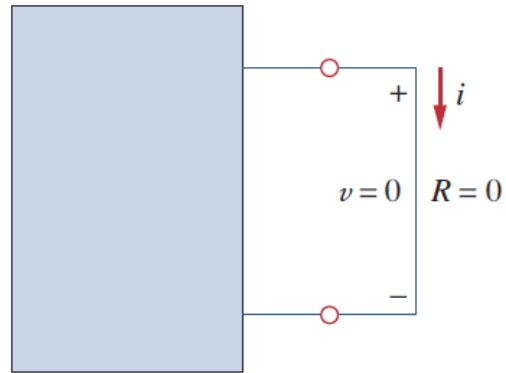

(a)

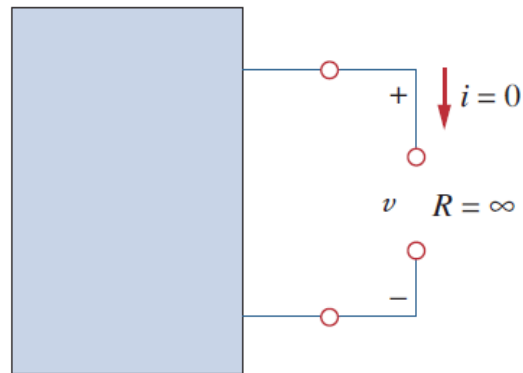

(b)


**Figure 2.2**

(a) Short circuit ( $R = 0$ ), (b) Open circuit ( $R = \infty$ ).




# Ideal Voltage Source

---

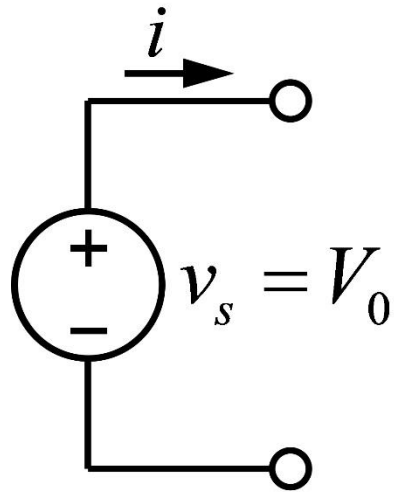

(a)

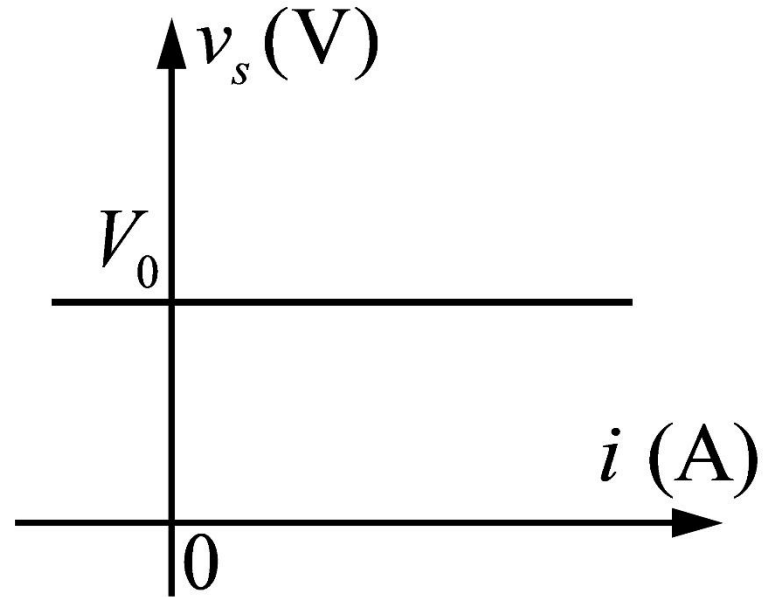

(b)

# Ideal Current Source

---

