


---

# Frequency Response

RC & RLC Circuits


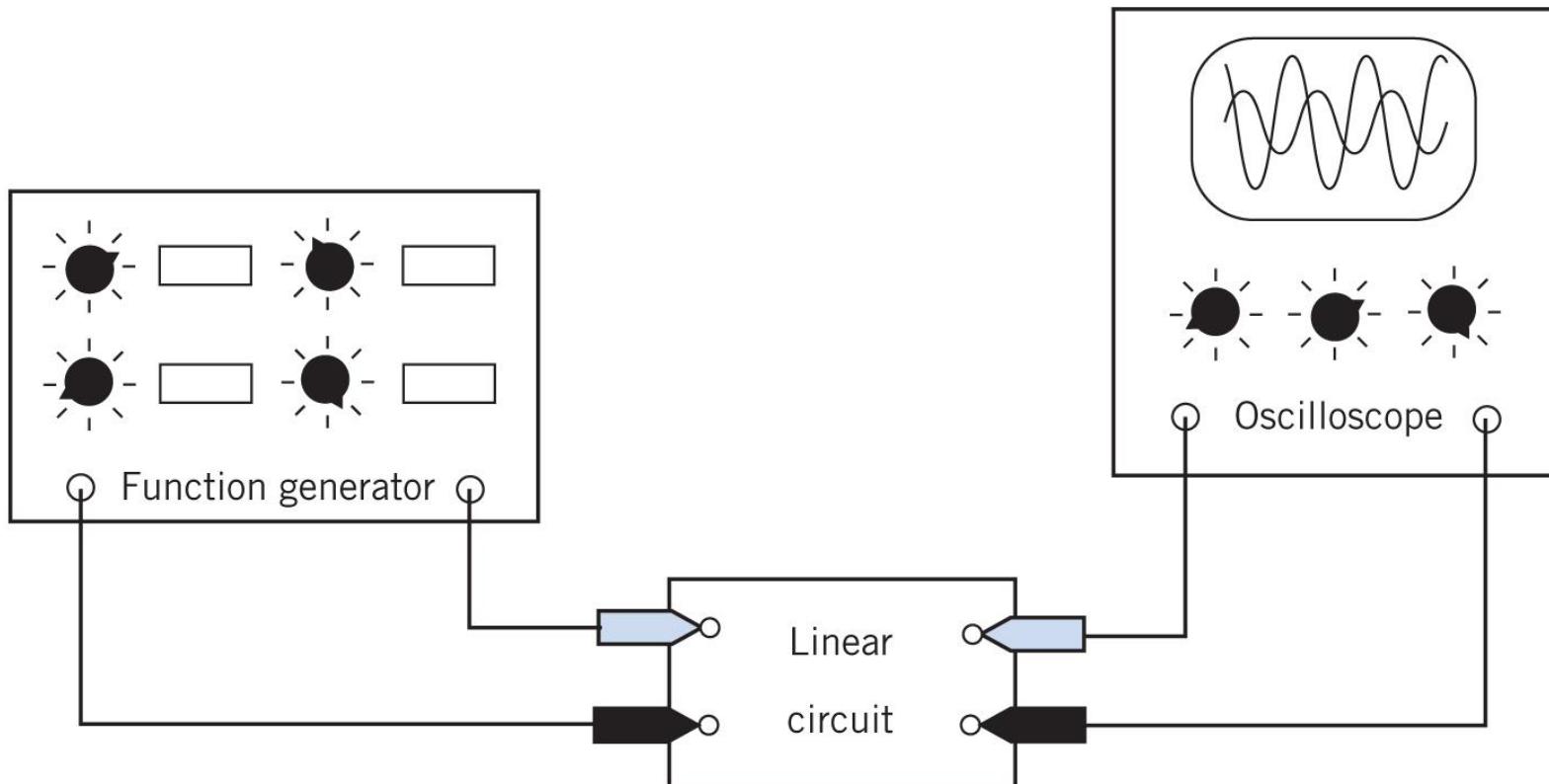
# Measuring Responses

- Define input and output
- Time response and frequency response




# Time Response and Frequency Response

---

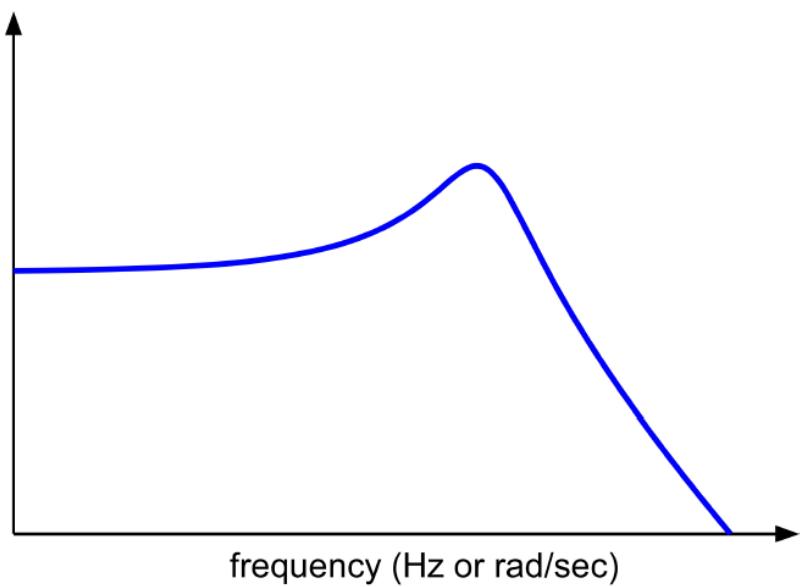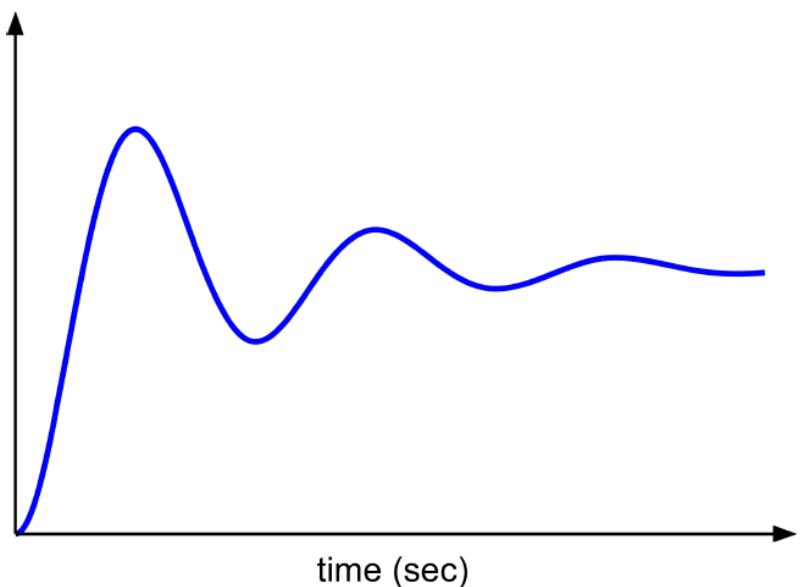


# Spectrum Analyzer

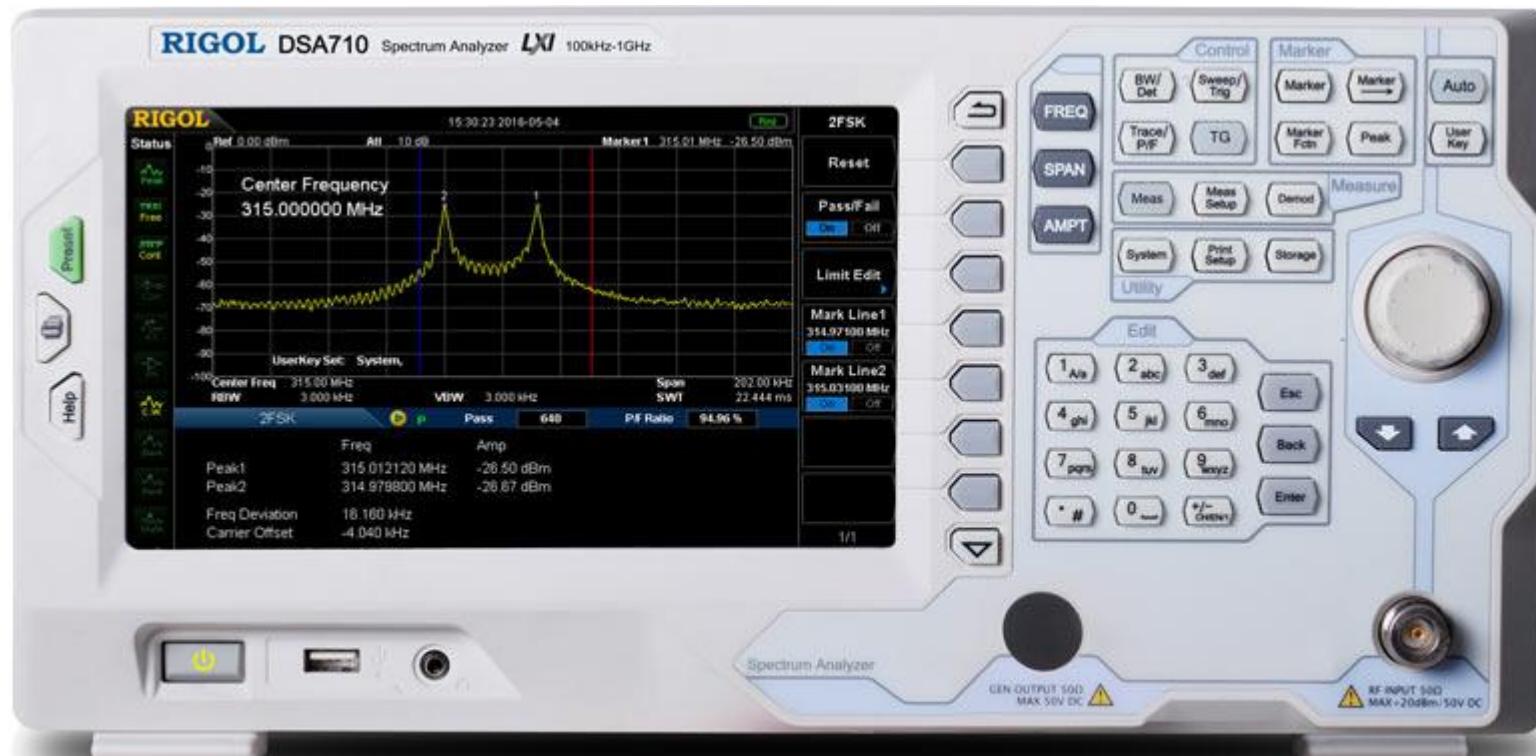

# Frequency Response

---

- Sinusoidal Input, Steady State

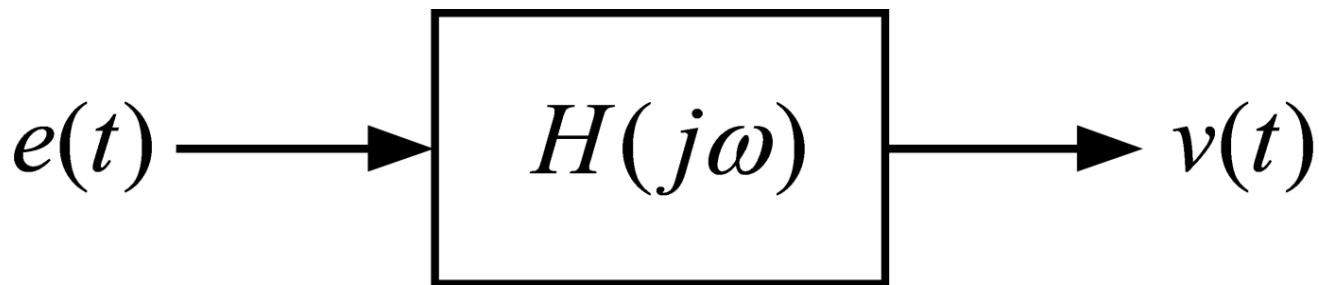


$$e(t) = A \cos(\omega t)$$

$$v(t) = A [ \quad ] \cos(\omega t + [ \quad ])$$



# Network Function

---

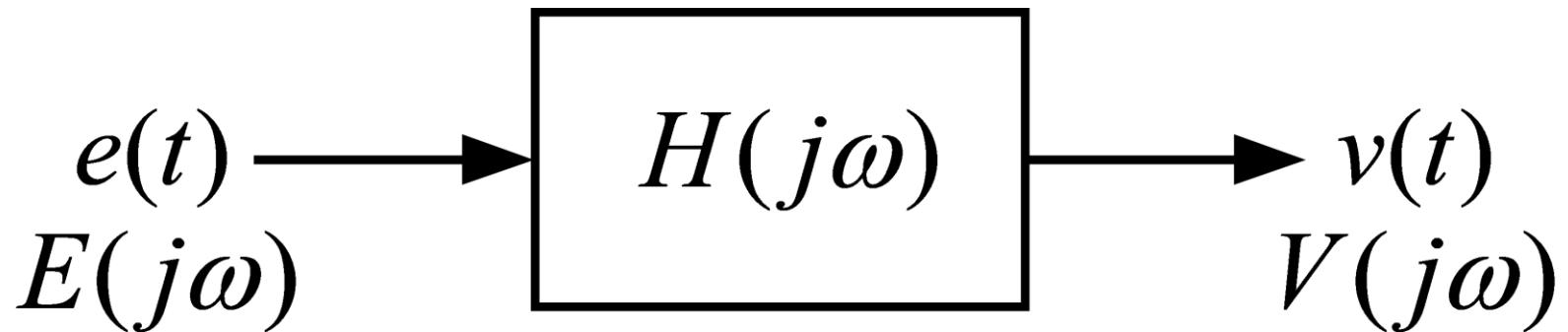

$$H(j\omega) = \frac{V(j\omega)}{E(j\omega)}$$

# Network Function

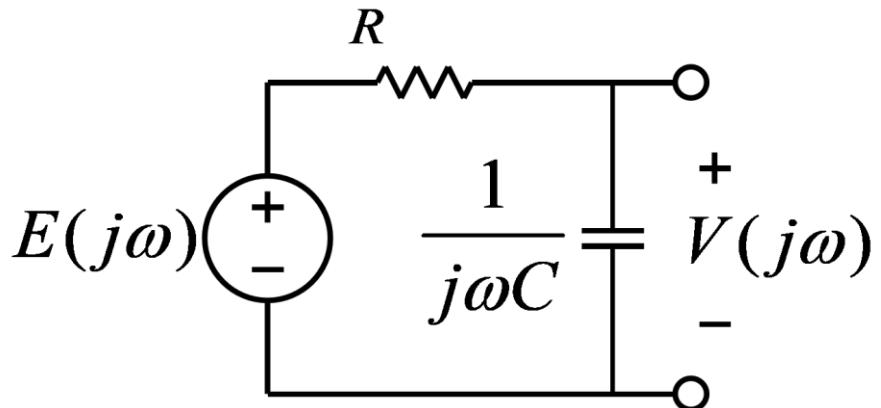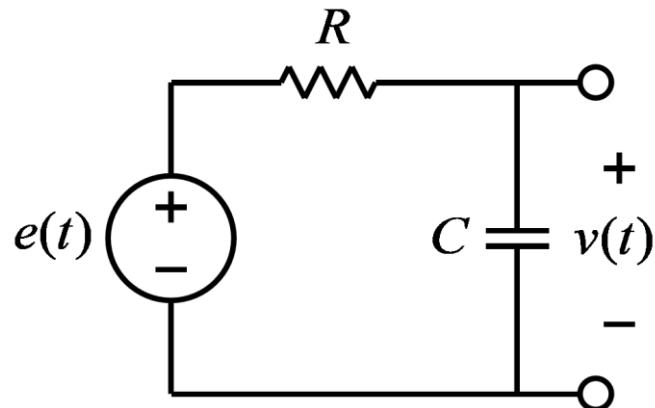

$$V(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} E(j\omega) = \frac{1}{j\omega RC + 1} E(j\omega)$$

$$H(j\omega) = \frac{V(j\omega)}{E(j\omega)} = \frac{1}{j\omega RC + 1}$$

# Network Function

---

$$V(j\omega) = \frac{V(j\omega)}{E(j\omega)} E(j\omega) = H(j\omega)E(j\omega)$$

$$= (|H(j\omega)| \angle H(j\omega)) E(j\omega)$$

$$e(t) = A \cos \omega t \Rightarrow E(j\omega) = A \angle 0^\circ$$

$$V(j\omega) = (|H(j\omega)| \angle H(j\omega)) A \angle 0^\circ$$


$$= A |H(j\omega)| \angle H(j\omega)$$

$$v(t) = A |H(j\omega)| \cos(\omega t + \angle H(j\omega))$$

# Frequency Response

---



- Sinusoidal Input, Steady State

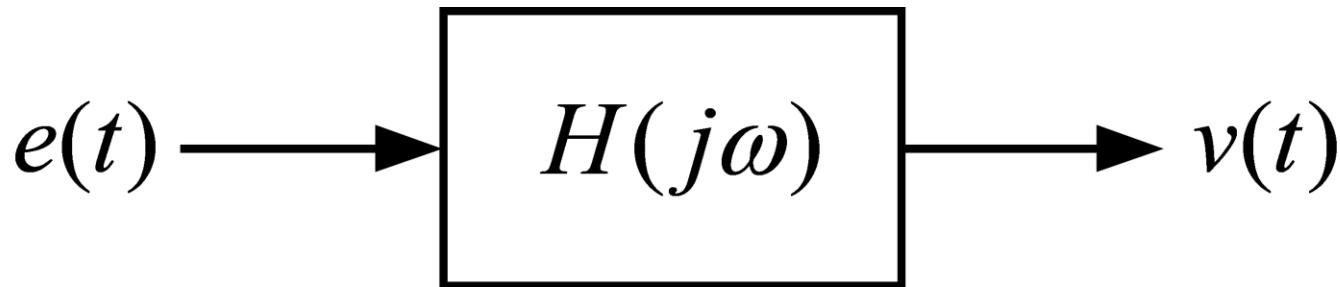

$$e(t) = A \cos(\omega t)$$

$$v(t) = A |H(j\omega)| \cos(\omega t + \angle H(j\omega))$$

# Low Pass RC Circuit

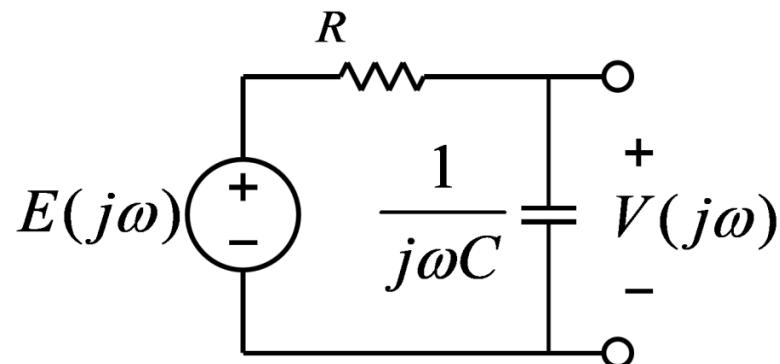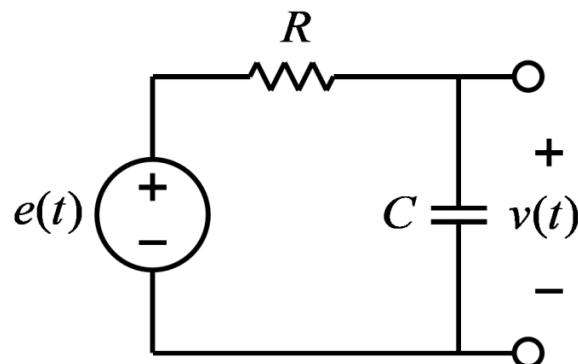

$$H(j\omega) = \frac{V(j\omega)}{E(j\omega)} = \frac{1}{j\omega RC + 1}$$



$$|H(j\omega)| = \left| \frac{1}{j\omega RC + 1} \right| = \frac{1}{\sqrt{(\omega RC)^2 + 1}}$$

$$\angle H(j\omega) = \angle \left( \frac{1}{j\omega RC + 1} \right) = \angle(1) - \angle(j\omega RC + 1) = -\tan^{-1}(\omega RC)$$

$$\text{Note: } \angle(a + jb) = \tan^{-1} \frac{b}{a}$$


$$R = 100\Omega, C = 0.001F$$

---

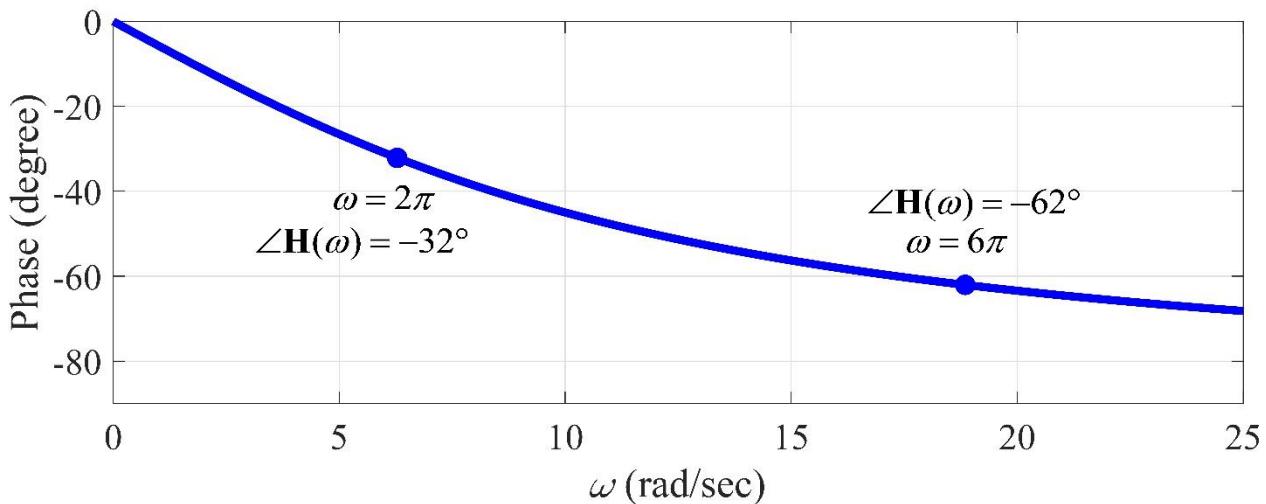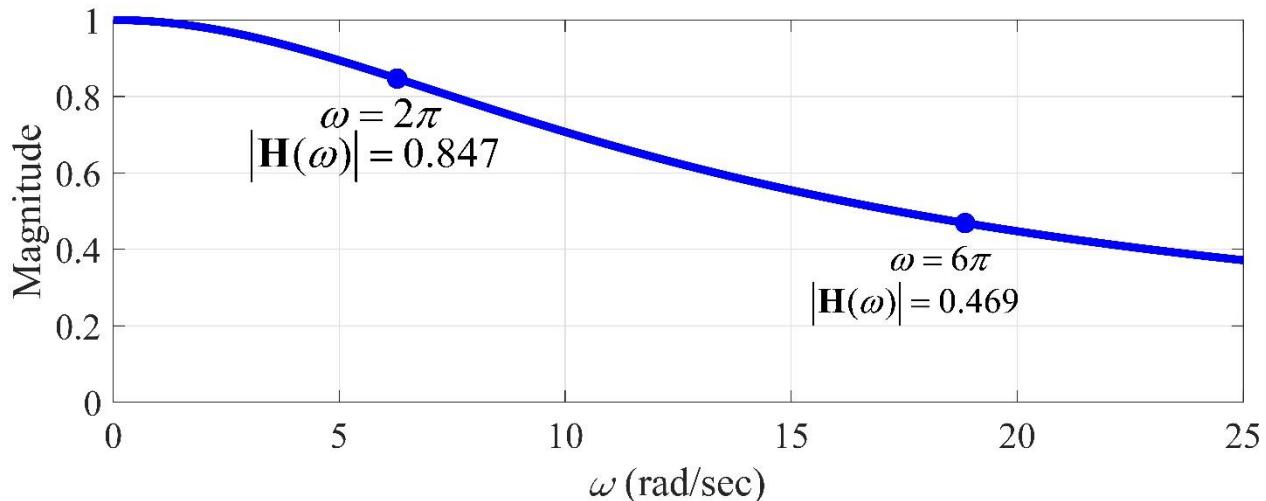


**1Hz**

---

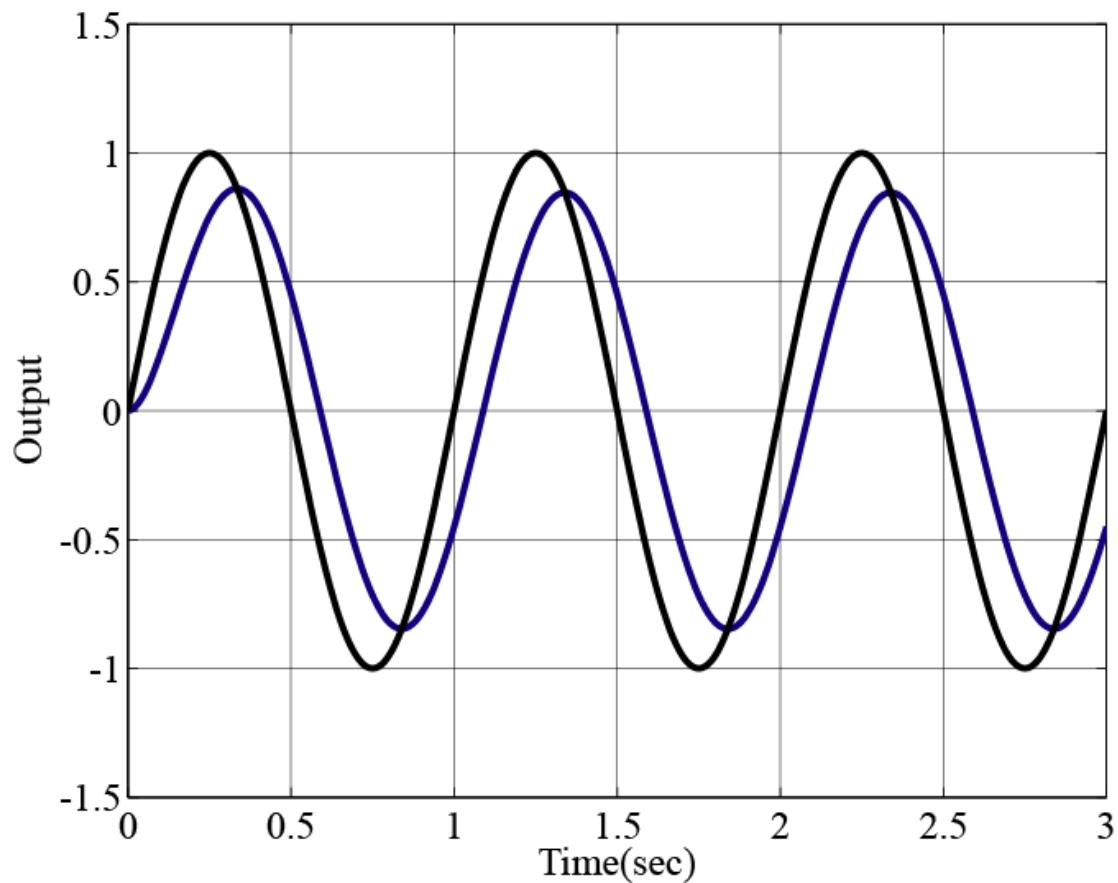

**3Hz**



---

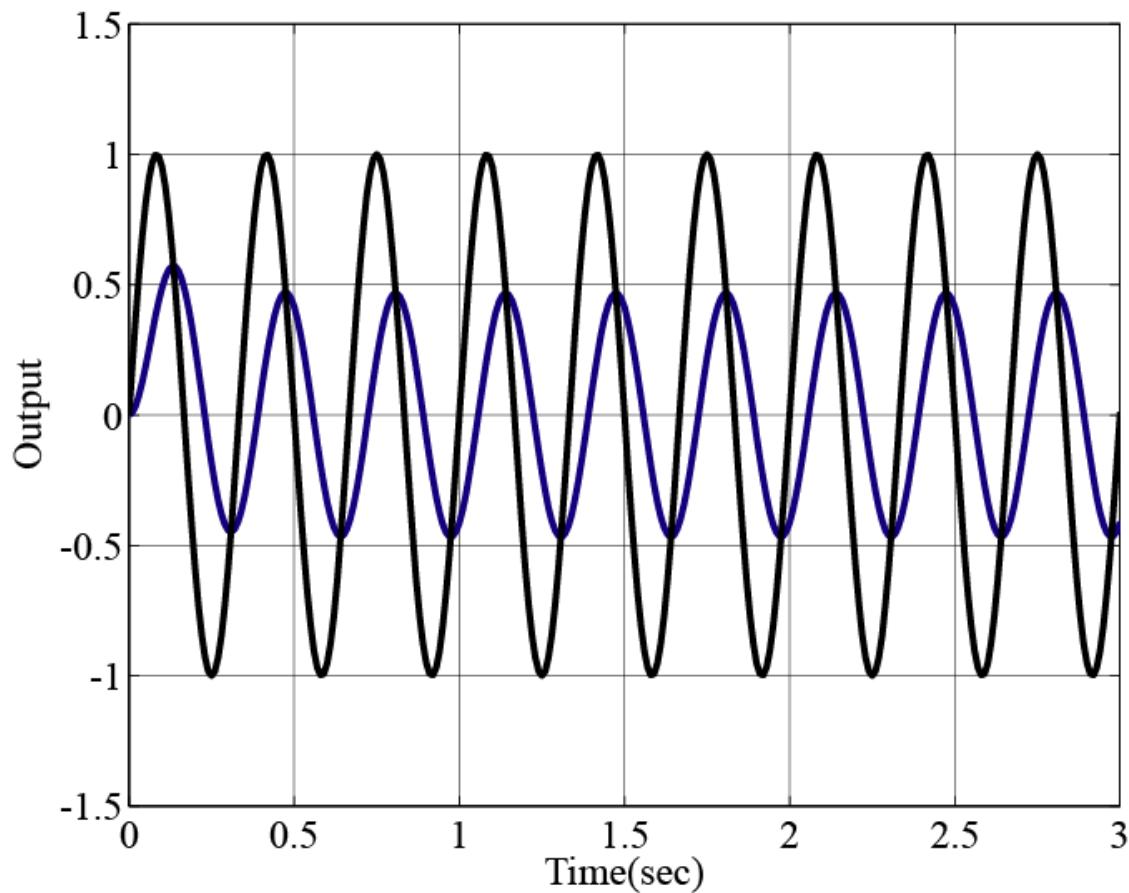
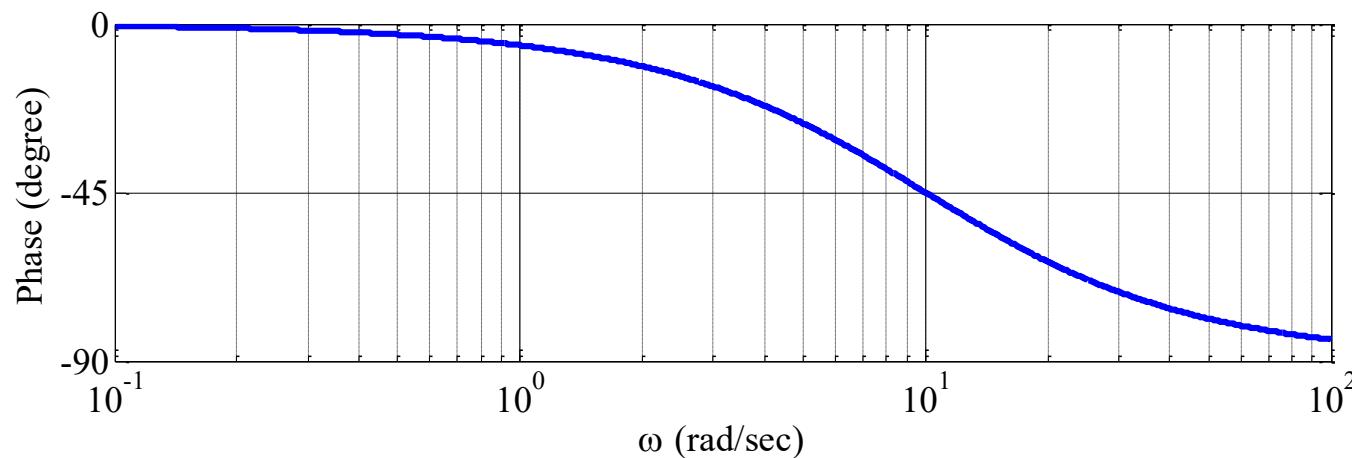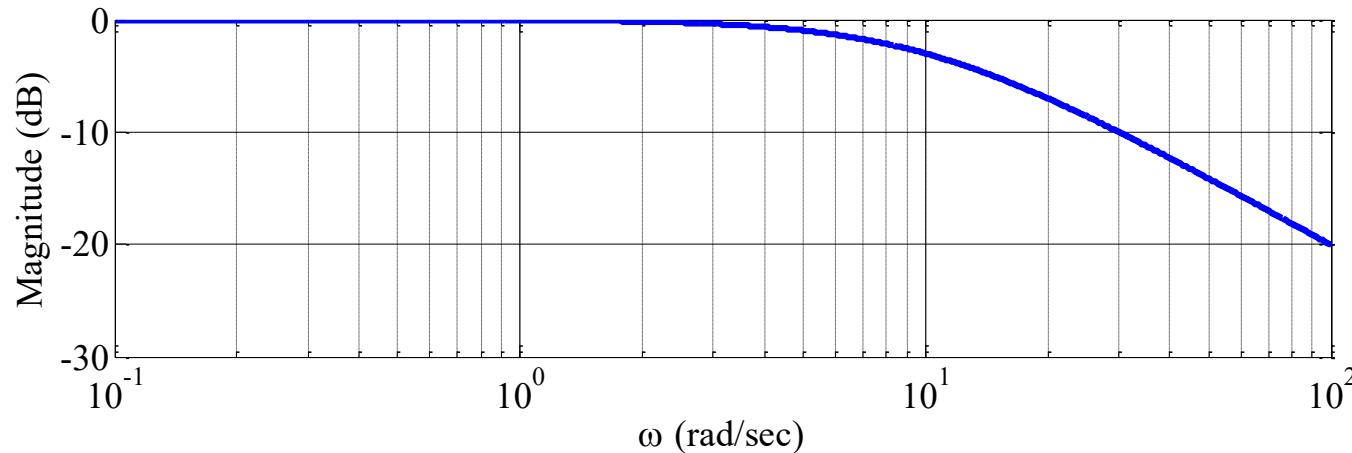
# Bode Plot

---

- dB(deci Bell):  $20\log(\text{magnitude})$




$$1/(s\tau + 1)$$

---


$$\left| \frac{1}{j\omega\tau + 1} \right|_{dB} = -20 \log_{10} |j\omega\tau + 1| \approx -20 \log_{10} 1 = 0 \quad \omega \ll 1/\tau$$

$$\left| \frac{1}{j\omega\tau + 1} \right|_{dB} = -20 \log_{10} |j\omega\tau + 1| \approx -20 \log_{10} |\omega\tau| \quad \omega \gg 1/\tau$$

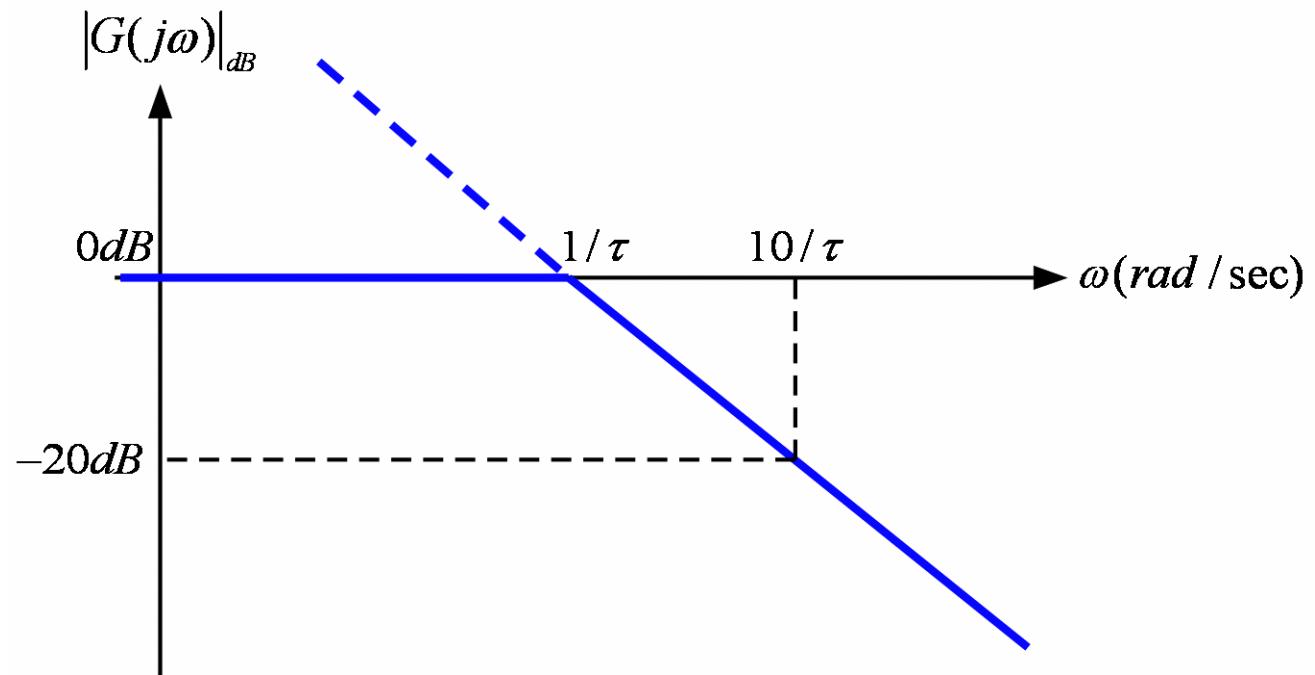

$$1/(s\tau + 1)$$

---

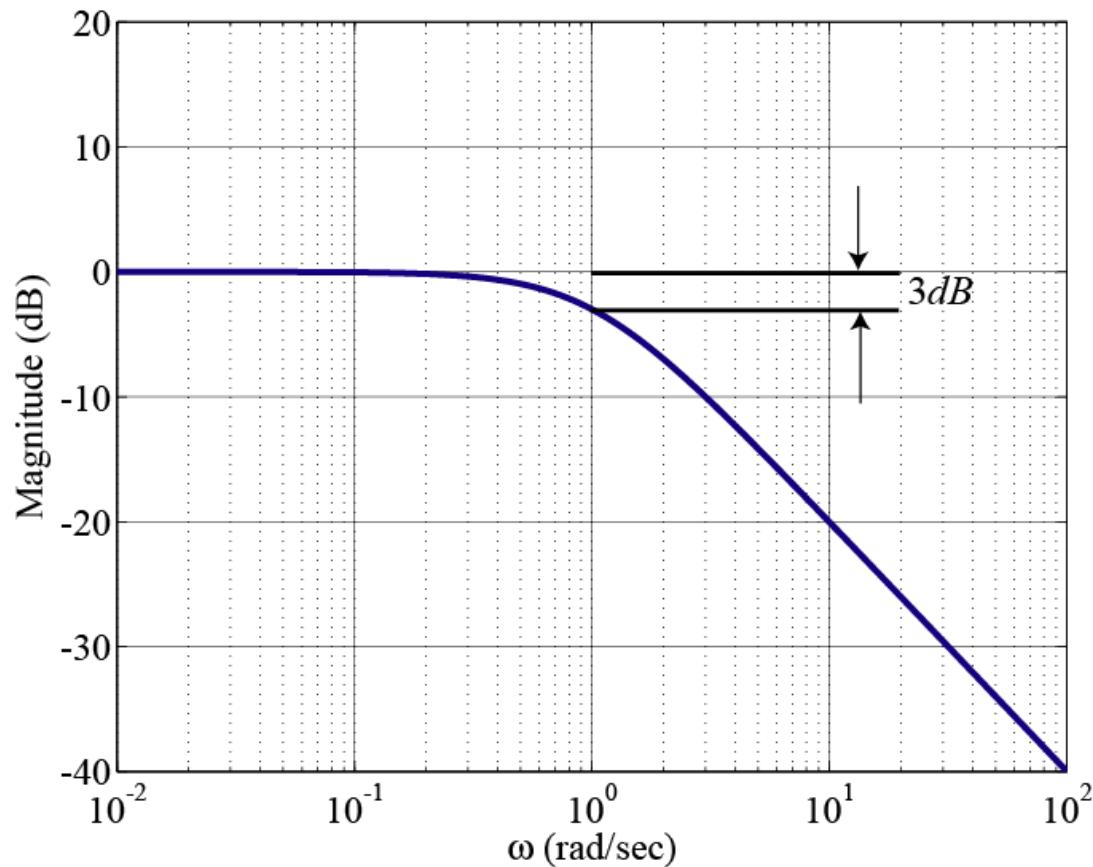


$$1/(s\tau + 1)$$

---

$$\angle\left(\frac{1}{j\omega\tau+1}\right) \approx -\angle 1 = 0^\circ \quad \omega \ll 1/\tau$$


$$\angle\left(\frac{1}{j\omega\tau+1}\right) = -\angle(j+1) = -45^\circ \quad \omega = 1/\tau$$
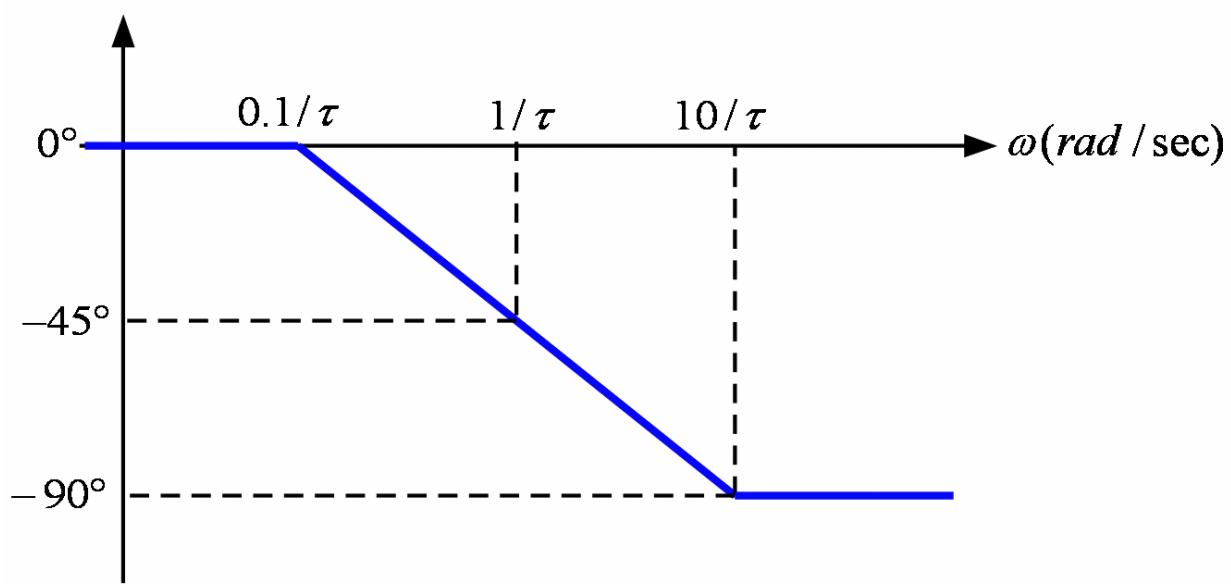
$$\angle\left(\frac{1}{j\omega\tau+1}\right) \approx -\angle(j\omega\tau) = -90^\circ \quad \omega \gg 1/\tau$$



$$1/(s\tau + 1)$$

---

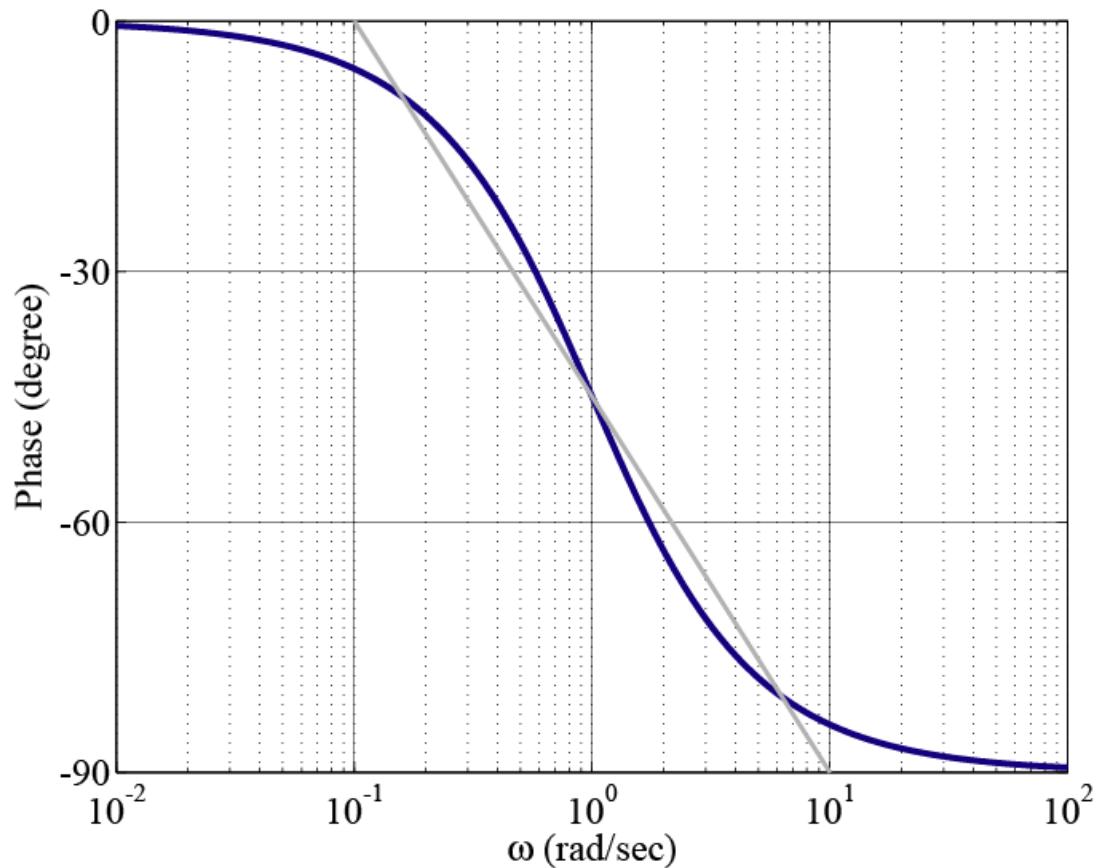

# Band Width, Cut Off Frequency

---

$$G(j\omega) = \frac{V(j\omega)}{E(j\omega)} = \frac{1}{j\omega RC + 1}$$


$$|G(j\omega)| = \left| \frac{1}{j\omega RC + 1} \right| = \frac{1}{\sqrt{(\omega RC)^2 + 1}}$$

$$\omega RC = 1 \Rightarrow |G(j\omega)| = \left| \frac{1}{j+1} \right| = \frac{1}{\sqrt{2}} \Rightarrow 20 \log_{10} \frac{1}{\sqrt{2}} = -3dB$$

$$\omega = \frac{1}{RC}$$

# High Pass RC Circuit

---

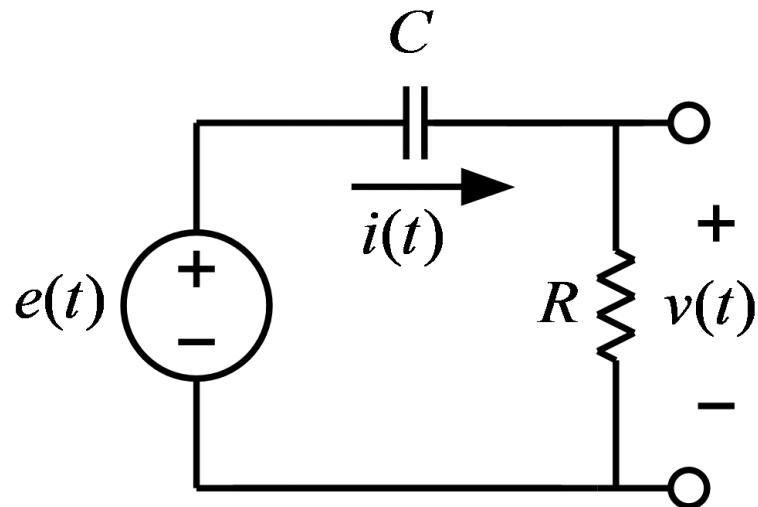

$$V(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} E(j\omega) = \frac{j\omega RC}{j\omega RC + 1} E(j\omega)$$

$$G(j\omega) = \frac{V(j\omega)}{E(j\omega)} = \frac{j\omega RC}{j\omega RC + 1}$$

---


$$G(j\omega) = \frac{V(j\omega)}{E(j\omega)} = \frac{j\omega RC}{j\omega RC + 1}$$

$$|G(j\omega)| = \left| \frac{j\omega RC}{j\omega RC + 1} \right| = \frac{\omega RC}{\sqrt{(\omega RC)^2 + 1}}$$



$$\angle G(j\omega) = \angle \left( \frac{j\omega RC}{j\omega RC + 1} \right) = 90^\circ - \tan^{-1} (\omega RC)$$

# Bode Plot

---

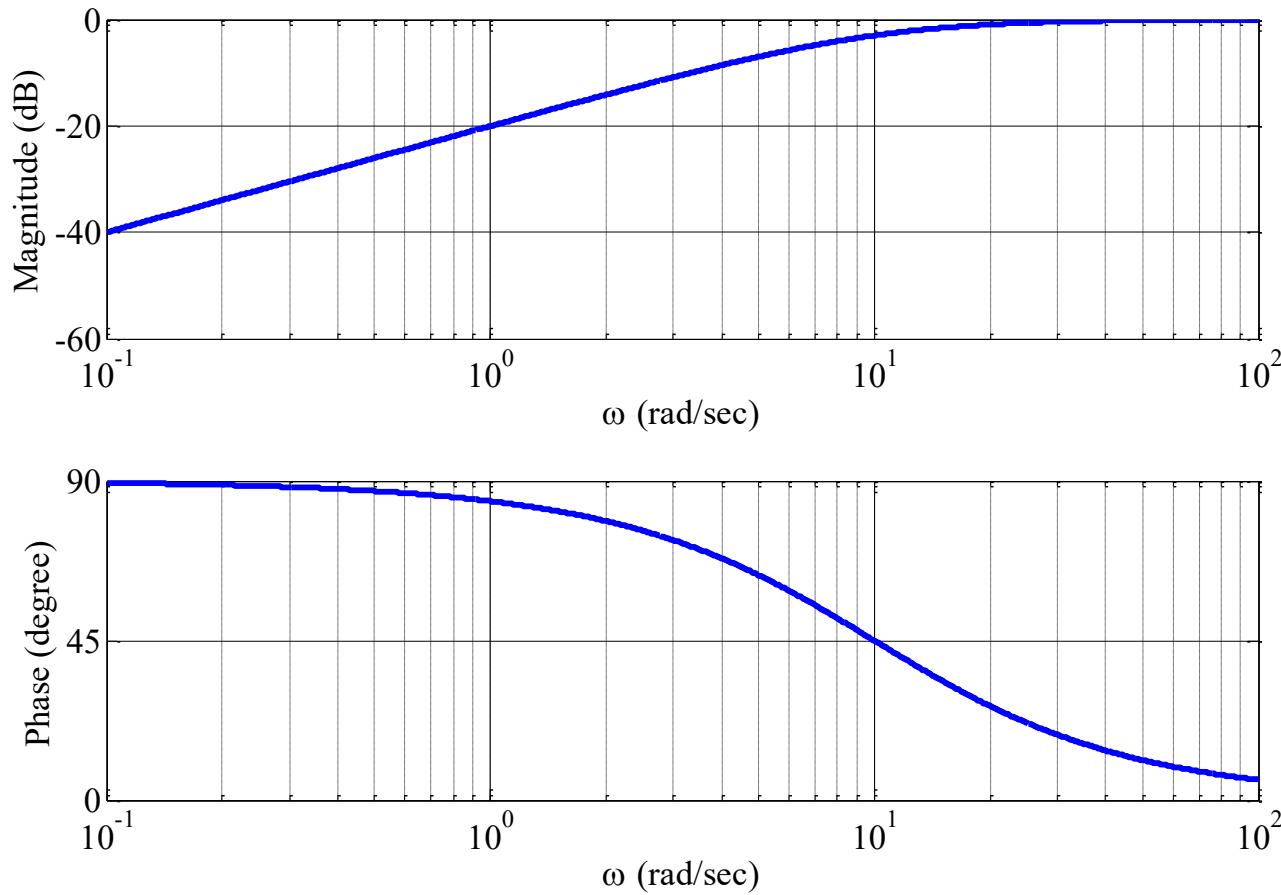

# RLC Circuit

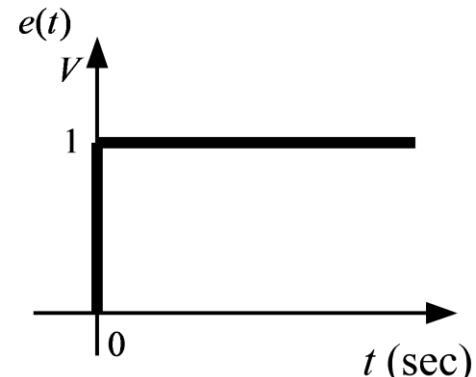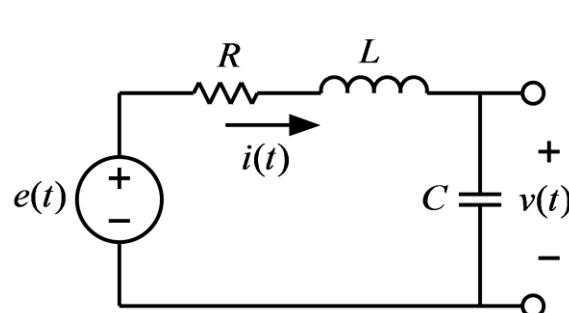

$$LC \frac{d^2v(t)}{dt^2} + RC \frac{dv(t)}{dt} + v(t) = e(t)$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0, s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0,$$


$$\text{damping ratio: } \zeta = \frac{\alpha}{\omega_0}, \alpha = \zeta\omega_0$$

---

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\zeta \omega_0 \pm \omega_0 \sqrt{\zeta^2 - 1}$$

$$\zeta < 1 : s = -\zeta \omega_0 \pm j \omega_0 \sqrt{1 - \zeta^2}$$
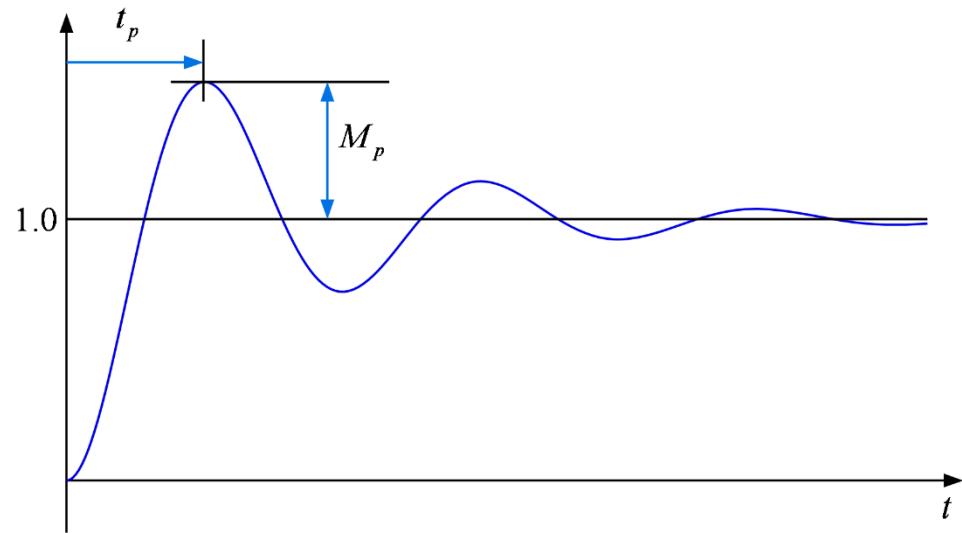
$$v(t) = -\frac{1}{\sqrt{1 - \left(\frac{\alpha}{\omega_0}\right)^2}} e^{-\alpha t} \cos(\omega_d t - \phi) + 1, \quad t \geq 0$$



### EXAMPLE 13.3-4 Network Function with Complex Poles

The network function of a second-order low-pass filter has the form

$$\mathbf{H}(\omega) = \frac{k \omega_0^2}{(j\omega)^2 + j2\zeta\omega_0\omega + \omega_0^2}$$

$$H(\omega) = \frac{k}{\left(j \frac{\omega}{\omega_0}\right)^2 + j2\zeta\left(\frac{\omega}{\omega_0}\right) + 1}$$

This network function depends on three parameters: the dc gain  $k$ ; the corner frequency  $\omega_0$ ; and the damping ratio  $\zeta$ . For convenience, we consider the case where  $k = 1$ . Then, using  $j^2 = -1$ , we can write the network function as

$$\mathbf{H}(\omega) = \frac{\omega_0^2}{\omega_0^2 - \omega^2 + j2\zeta\omega_0\omega}$$

Determine the asymptotic magnitude Bode plot of the second-order low-pass filter when the dc gain is 1.

### Solution

The denominator of  $\mathbf{H}(\omega)$  contains a new factor, one that involves  $\omega^2$ . The asymptotic Bode plot is based on the approximation

$$(\omega_0^2 - \omega^2) + j2\zeta\omega_0\omega \cong \begin{cases} \omega_0^2 & \omega < \omega_0 \\ -\omega^2 & \omega > \omega_0 \end{cases}$$

Using this approximation, we can express  $\mathbf{H}(\omega)$  as

$$\mathbf{H}(\omega) \cong \begin{cases} 1 & \omega < \omega_0 \\ -\frac{\omega_0^2}{\omega^2} & \omega > \omega_0 \end{cases}$$


The logarithmic gain is

$$20 \log_{10} |\mathbf{H}(\omega)| \cong \begin{cases} 0 & \omega < \omega_0 \\ 40 \log_{10} \omega_0 - 40 \log_{10} \omega & \omega > \omega_0 \end{cases}$$

The asymptotic magnitude Bode plot is shown in Figure 13.3-10. The actual magnitude Bode plot and the actual phase Bode plot are shown in Figure 13.3-11. The asymptotic Bode plot is a good approximation to the actual Bode plot when  $\omega \ll \omega_0$  or  $\omega \gg \omega_0$ . Near  $\omega = \omega_0$ , the asymptotic Bode plot deviates from the actual Bode plot. At  $\omega = \omega_0$ , the value of the asymptotic Bode plot is 0 dB, whereas the value of the actual Bode plot is

$$H(\omega_0) = \frac{1}{2\zeta}$$

As this equation and Figure 13.3-11 both show, the deviation between the actual and asymptotic Bode plot near  $\omega = \omega_0$  depends on  $\zeta$ . The frequency  $\omega_0$  is called the *corner frequency*. The slope of the asymptotic Bode plot decreases by 40 dB/decade as the frequency increases past  $\omega = \omega_0$ . In terms of the asymptotic Bode plot, the denominator of this network function acts like two poles at  $p = \omega_0$ . If this factor were to appear in the numerator of a network function, it would act like two zeros at  $z = \omega_0$ . The slope of the asymptotic Bode plot would increase by 40 dB/decade as the frequency increased past  $\omega = \omega_0$ .

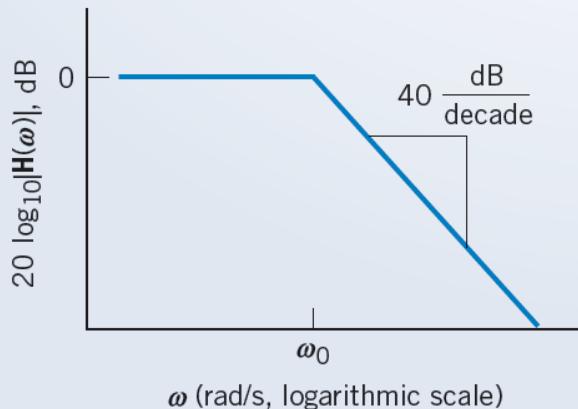

**FIGURE 13.3-10** The asymptotic magnitude Bode plot of the second-order low-pass filter when the dc gain is 1.

$$1/\left[\left(j\omega/\omega_0\right)^2 + \left(2\zeta j\omega/\omega_0\right) + 1\right]$$

---

$$\left[\left(j\omega/\omega_0\right)^2 + \left(j2\zeta\omega/\omega_0\right) + 1\right]$$

$$= \left[\left(j\omega/\omega_0\right) + \zeta + \sqrt{\zeta^2 - 1}\right] \left[\left(j\omega/\omega_0\right) + \zeta - \sqrt{\zeta^2 - 1}\right]$$

real root:  $1 < \zeta$

double root:  $\zeta = 1$


complex root:  $\zeta < 1$


$$1/\left[\left(j\omega/\omega_0\right)^2 + \left(2\zeta j\omega/\omega_0\right) + 1\right]$$


---


$$\left| \frac{1}{\left(j\omega/\omega_0\right)^2 + \left(2\zeta j\omega/\omega_0\right) + 1} \right|_{dB} \approx -20 \log_{10} 1 = 0 \quad \omega \ll \omega_0$$
  

$$\left| \frac{1}{\left(j\omega/\omega_0\right)^2 + \left(2\zeta j\omega/\omega_0\right) + 1} \right|_{dB} \approx -20 \log_{10} \left| \left(\omega/\omega_0\right)^2 \right| \quad \omega \gg \omega_0$$

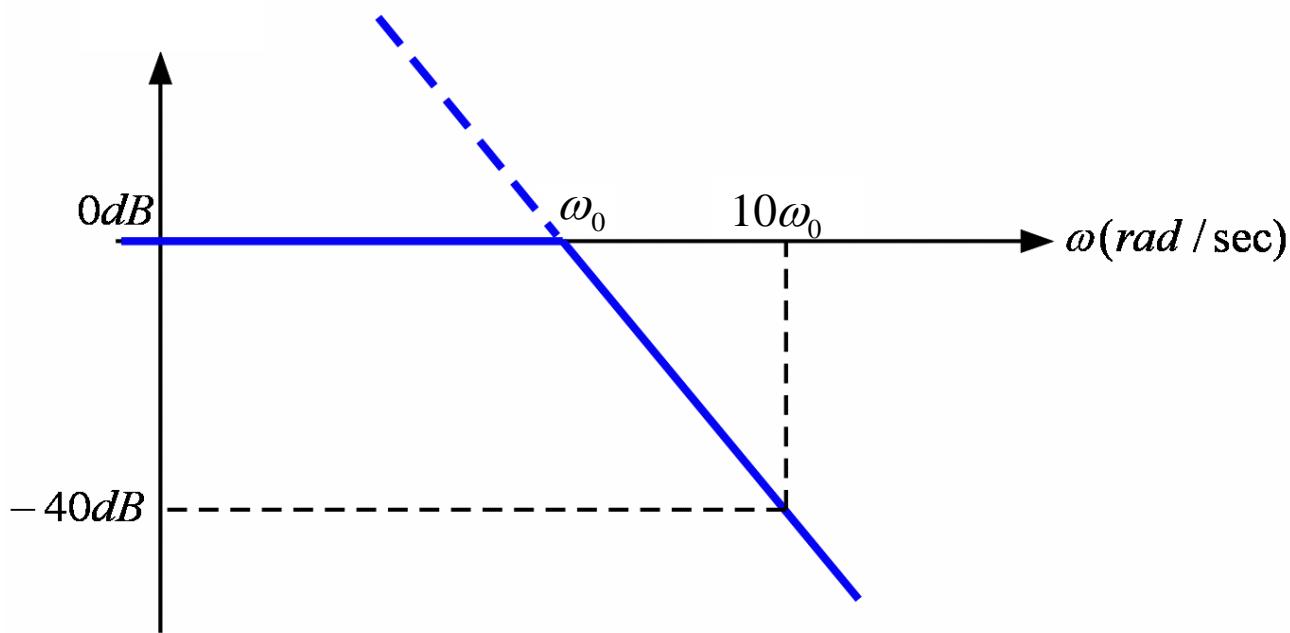

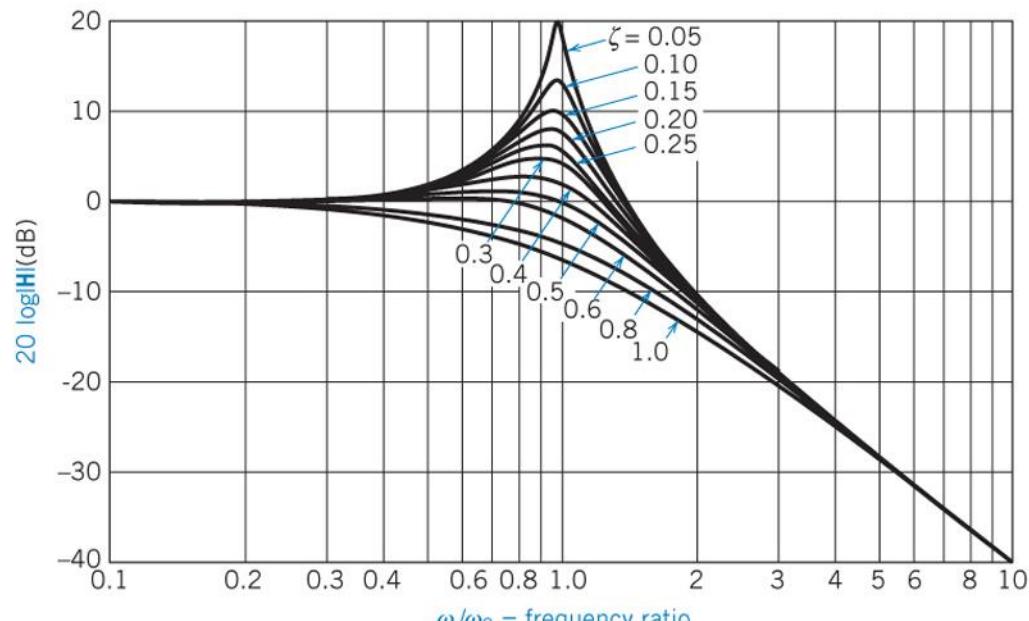


(a)

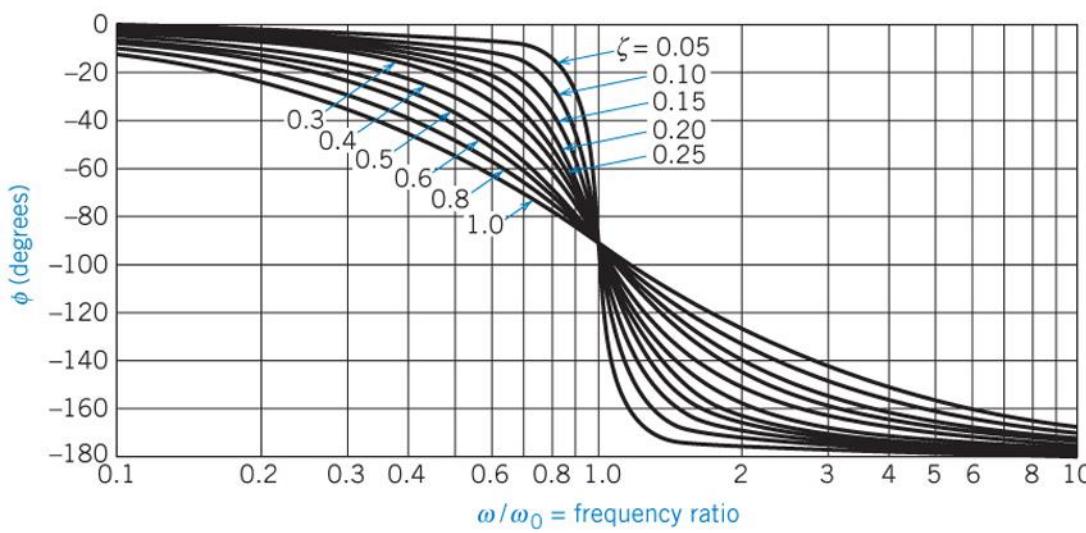

(b)

# Low Pass RLC Circuit

---

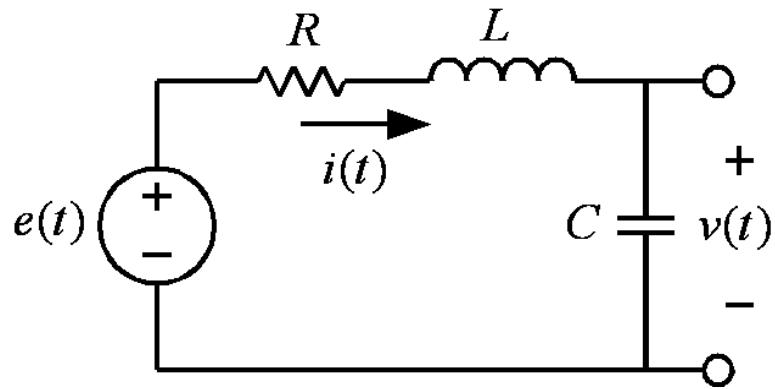

$$V(j\omega) = \frac{\frac{1}{j\omega C}}{j\omega L + R + \frac{1}{j\omega C}} E(j\omega) = \frac{1}{(j\omega)^2 LC + (j\omega)RC + 1} E(j\omega)$$

# Low Pass RLC Circuit

---

$$V(j\omega) = \frac{\frac{1}{j\omega C}}{j\omega L + R + \frac{1}{j\omega C}} E(j\omega) = \frac{1}{(j\omega)^2 LC + (j\omega)RC + 1} E(j\omega)$$

$$H(j\omega) = \frac{V(j\omega)}{E(j\omega)} = \frac{1}{(j\omega)^2 LC + (j\omega)RC + 1} = \frac{1/(LC)}{(j\omega)^2 + (R/L)(j\omega) + 1/(LC)}$$

$$H(j\omega) = \frac{\omega_0^2}{(j\omega)^2 + 2\alpha(j\omega) + \omega_0^2}$$

$$\alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}, \zeta = \frac{\alpha}{\omega_0}$$

---

$$R = 100\Omega, L = 100mH, C = 0.1\mu F$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-1}10^{-7}}} = 10^4$$

$$\alpha = \frac{R}{2L} = \frac{100}{2 \times 10^{-1}} = 500, \zeta = \frac{500}{10000} = 0.05$$

$$|H(j\omega_0)| = \frac{1}{2\zeta} = 10 = 20dB$$

