

---

# OP Amp Basic Circuits 2

Voltage Follower

Integrator


Active Low-Pass Filter

Differentiator

# Voltage Follower/Impedance Buffer


---

- Non-inverting amplifier: Gain = 1

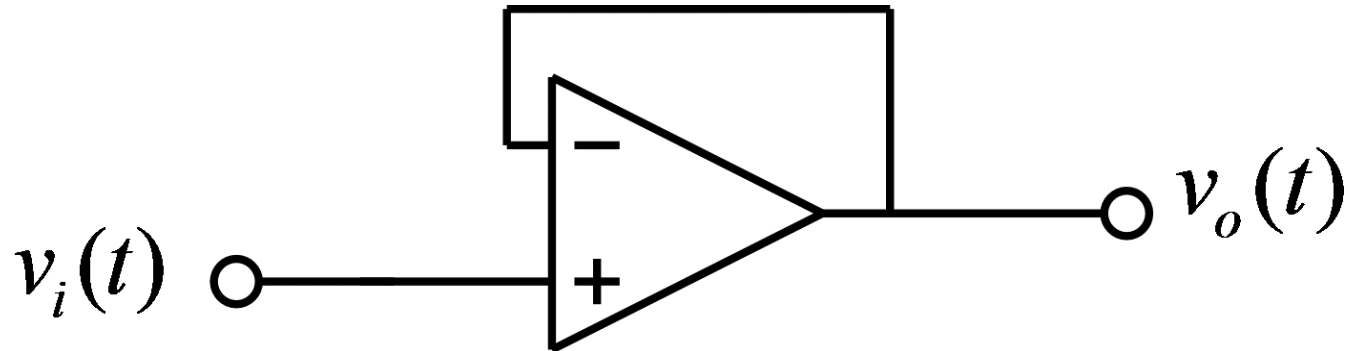


# RC Low-Pass Filter

---

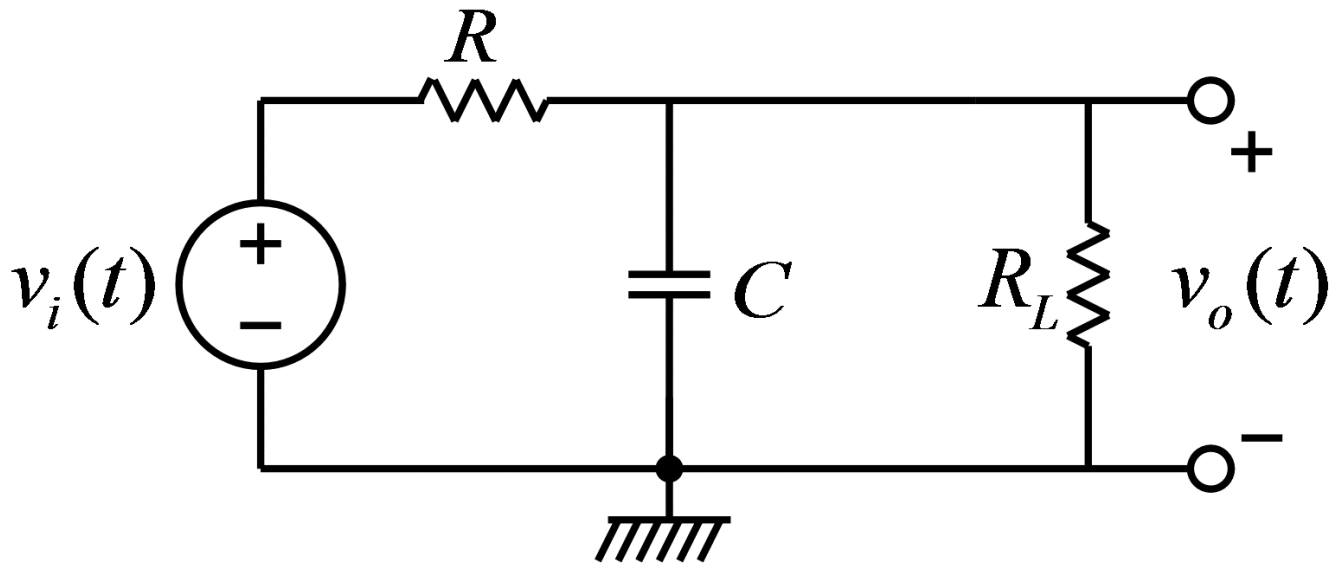


# Buffered RC Low-Pass Filter

---

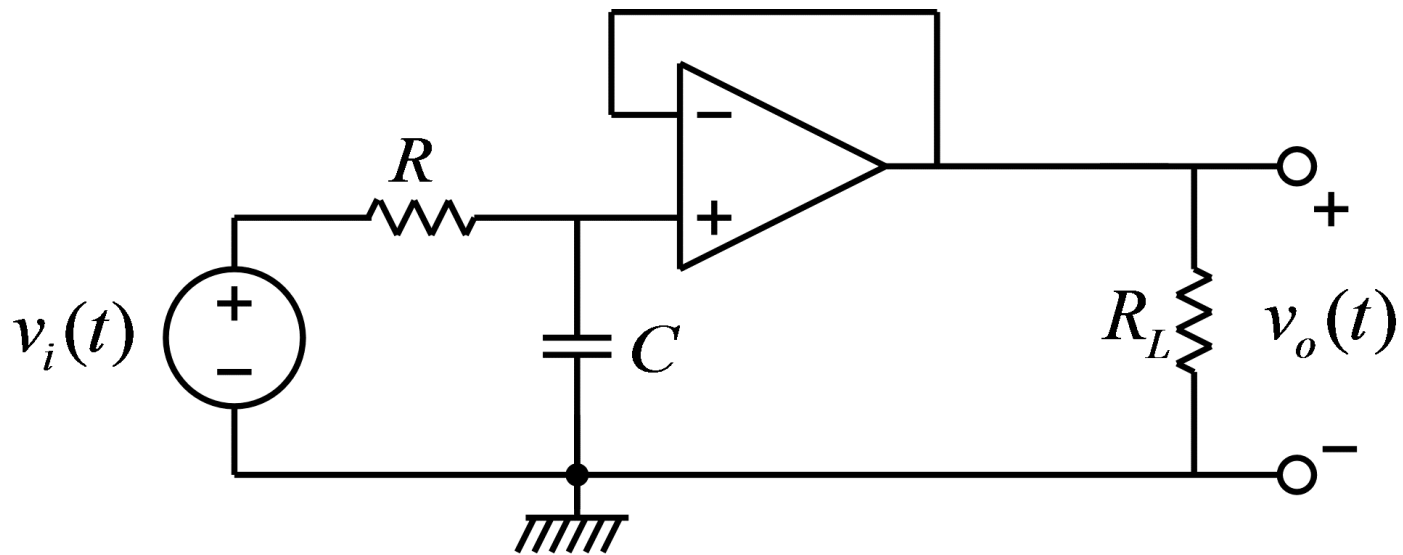

# Integrator

---

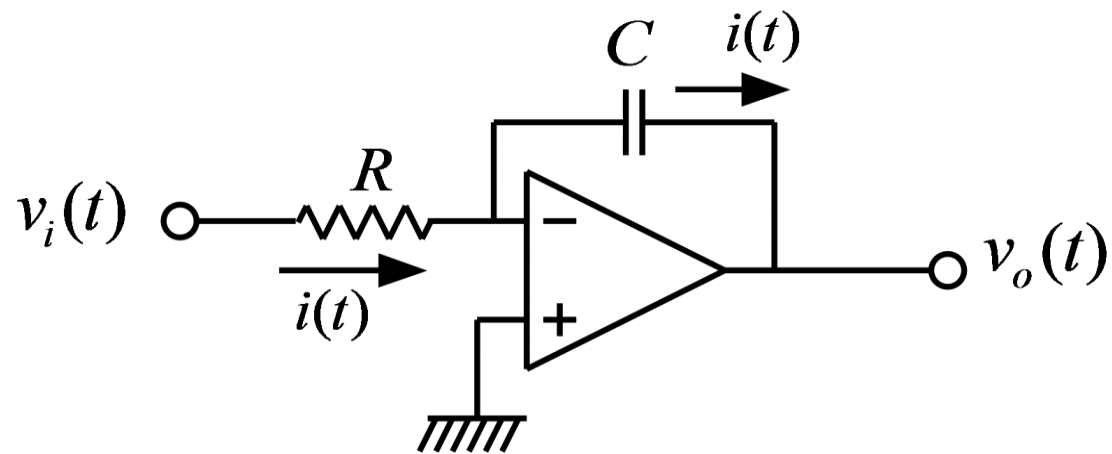


$$i(t) = \frac{v_i(t)}{R}$$

$$v_o(t) = -\frac{1}{C} \int_0^t i(\tau) d\tau + v_o(0) = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau + v_o(0)$$

# Active Low-Pass Filter


---

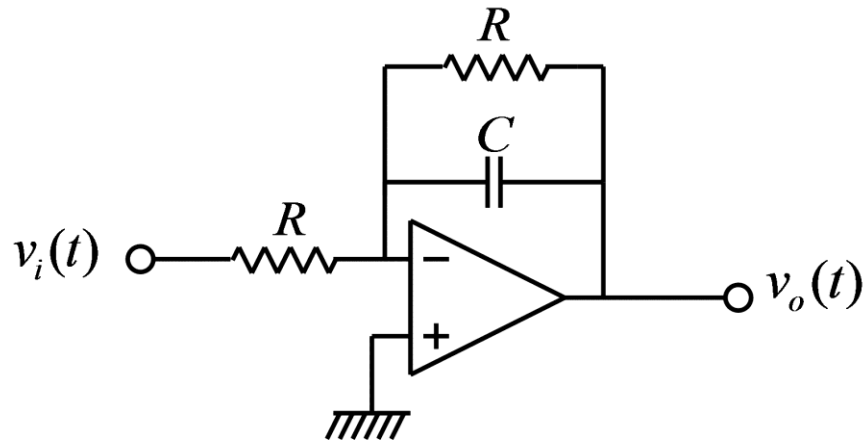

$$G(j\omega) = -\frac{\left( R \parallel \frac{1}{j\omega C} \right)}{R} = -\frac{1}{R} \left( \frac{\frac{R}{j\omega C}}{R + \frac{1}{j\omega C}} \right) = -\frac{1}{j\omega RC + 1}$$

# Differentiator

---

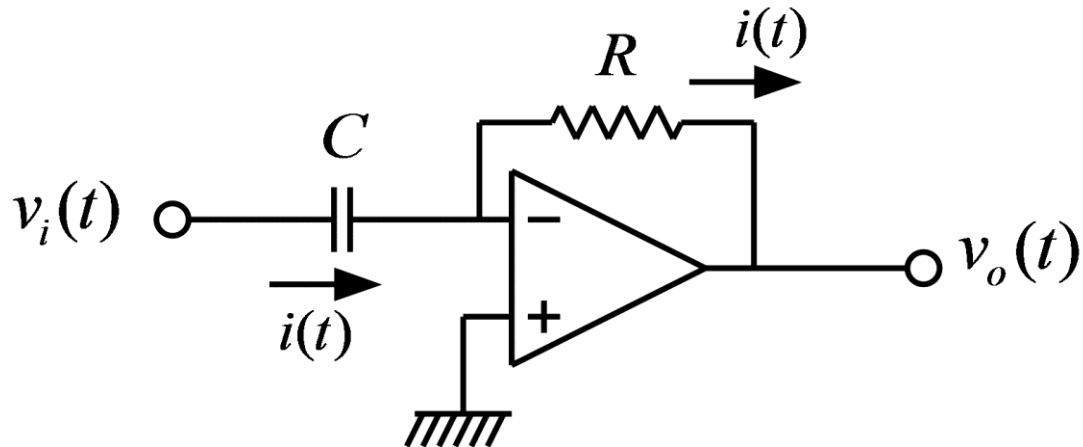

$$i(t) = C \frac{dv_i(t)}{dt}$$

$$v_o(t) = -Ri(t) = -RC \frac{dv_i(t)}{dt}$$

$$v_i(t) = A \cos \omega t \Rightarrow v_o(t) = RCA\omega \sin \omega t$$