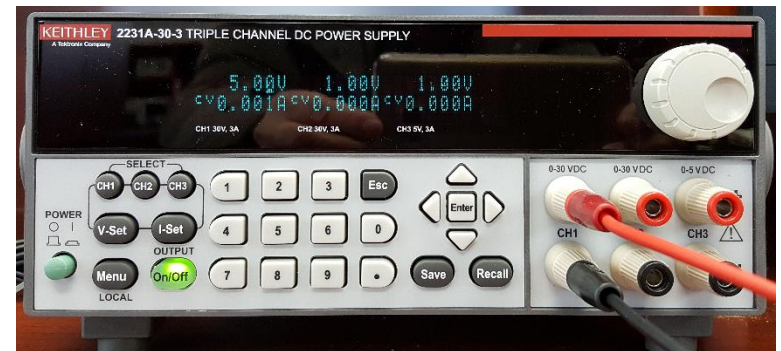
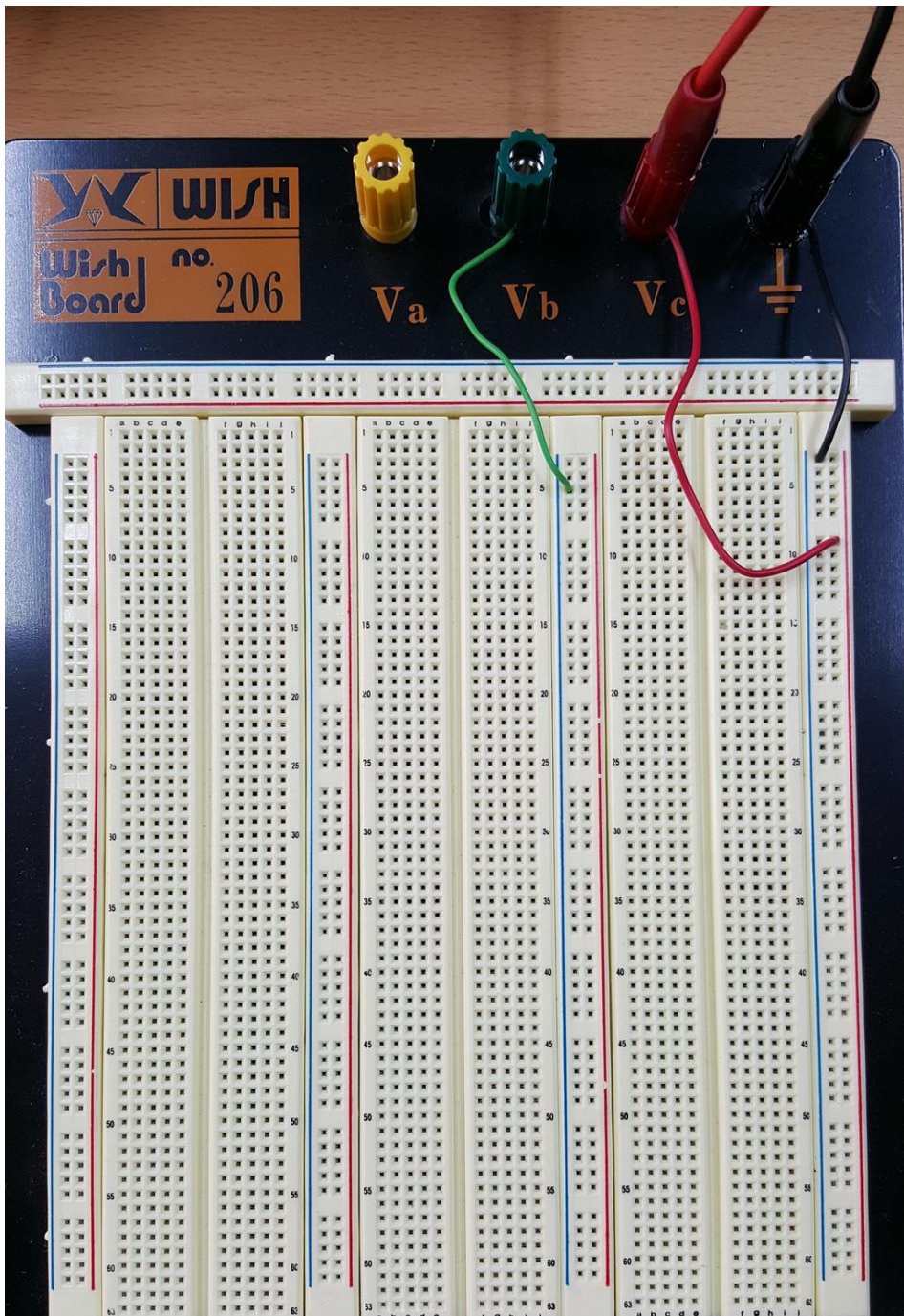
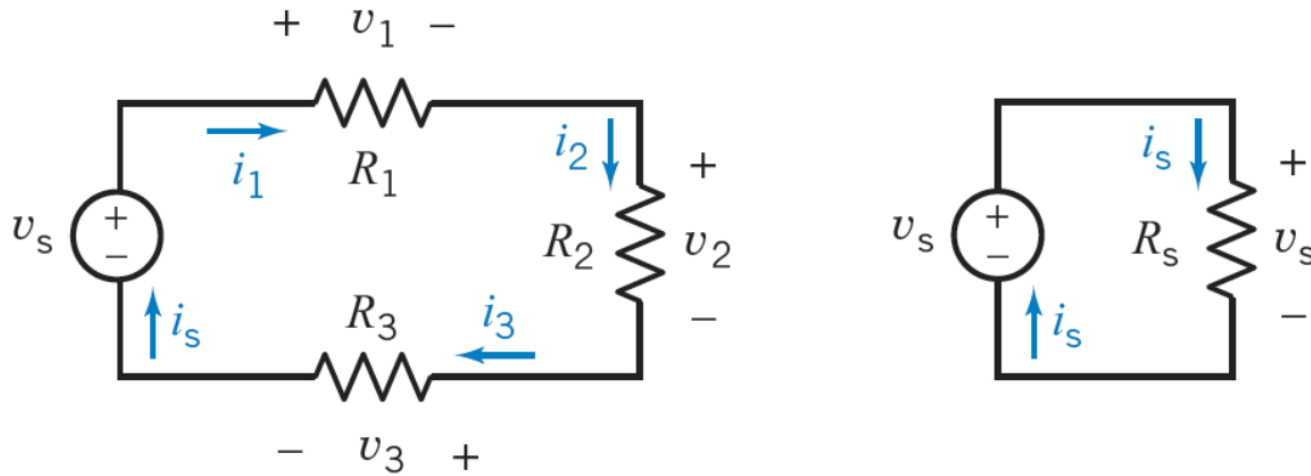

Optoelectronics Lab

Series & Parallel Resistors
Thevenin's Theorem

Breadboard



Series Resistors



$$v_1 + v_2 + v_3 - v_s = 0$$

$$R_1 i_1 + R_2 i_2 + R_2 i_3 - v_s = 0 \Rightarrow R_1 i_1 + R_2 i_1 + R_2 i_1 = v_s$$

$$i_1 = \frac{v_s}{R_1 + R_2 + R_3}$$

$$i_s = \frac{v_s}{R_1 + R_2 + R_3}$$

$$i_s = \frac{v_s}{R_s}$$

$$R_s = R_1 + R_2 + R_3$$


Voltage Division

$$v_1 = R_1 i_S = \frac{R_1}{R_1 + R_2 + R_3} v_S$$

$$v_2 = R_2 i_S = \frac{R_2}{R_1 + R_2 + R_3} v_S$$

$$v_3 = R_3 i_S = \frac{R_3}{R_1 + R_2 + R_3} v_S$$

Parallel Resistors

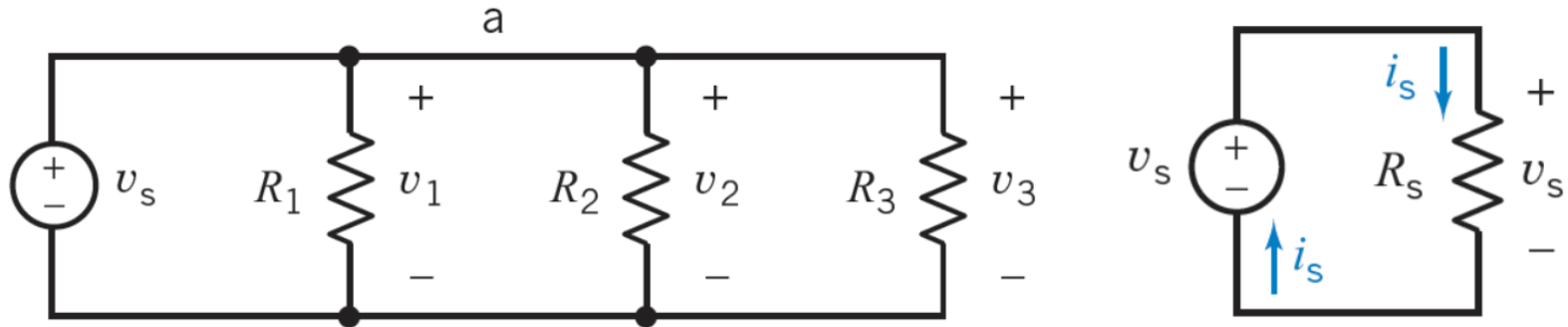

$$i_s = i_1 + i_2 + i_3 = \frac{v_s}{R_1} + \frac{v_s}{R_2} + \frac{v_s}{R_3} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v_s$$

$$i_s = \left(\frac{1}{R_s} \right) v_s$$

$$\frac{1}{R_s} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow R_s = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

Current Division

$$i_1 = \frac{v_S}{R_1} = \frac{1}{R_1} R_S i_S = \frac{\frac{1}{R_1}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} i_S$$

$$i_2 = \frac{v_S}{R_2} = \frac{1}{R_2} R_S i_S = \frac{\frac{1}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} i_S$$

$$i_3 = \frac{v_S}{R_3} = \frac{1}{R_3} R_S i_S = \frac{\frac{1}{R_3}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} i_S$$

$$\frac{1}{R_S} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_S = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} = \frac{R_1 R_2}{R_1 + R_2}$$

Thevenin's Theorem

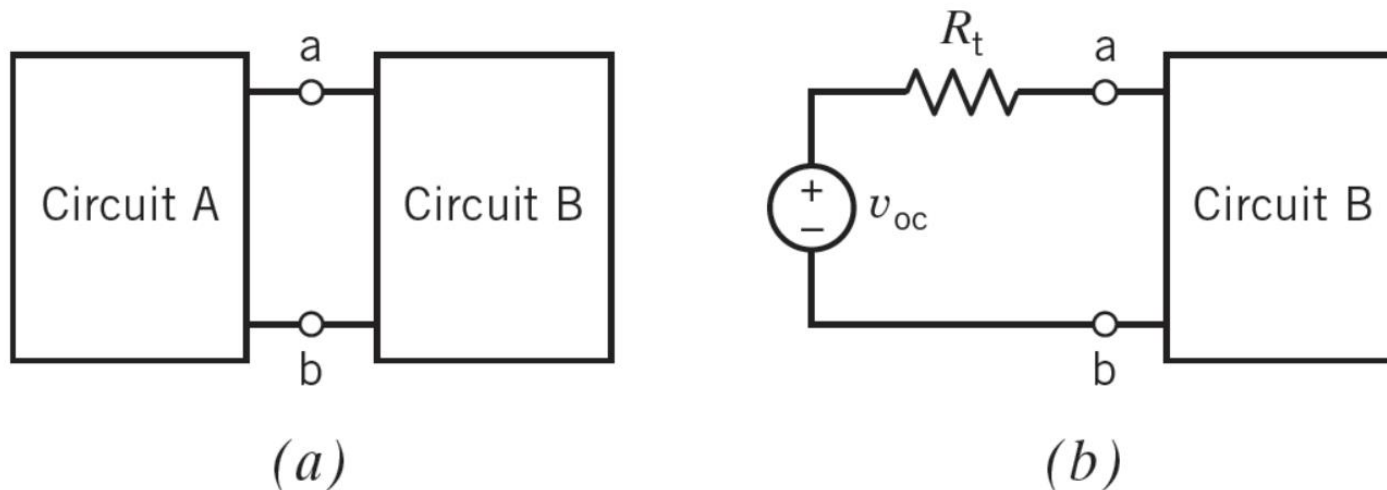


FIGURE 5.4-2 (a) A circuit partitioned into two parts: circuit A and circuit B. (b) Replacing circuit A by its Thévenin equivalent circuit.


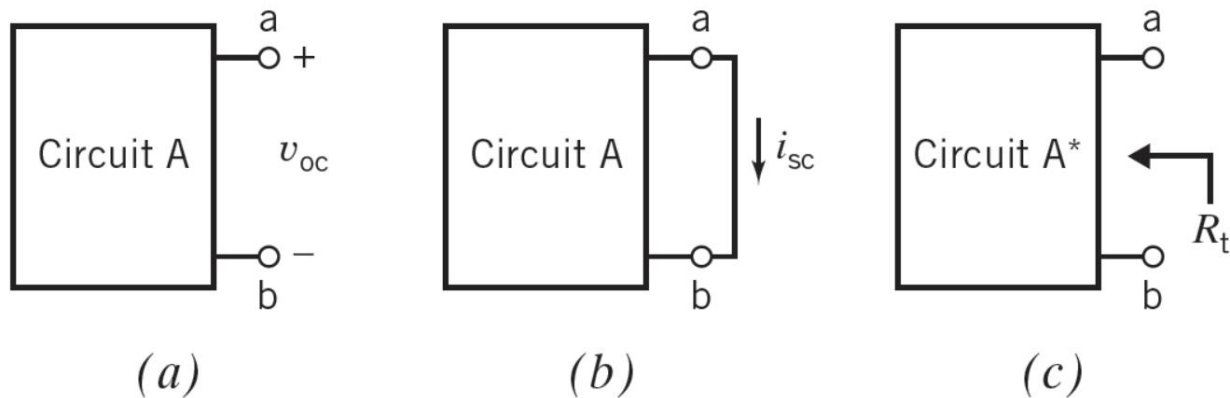
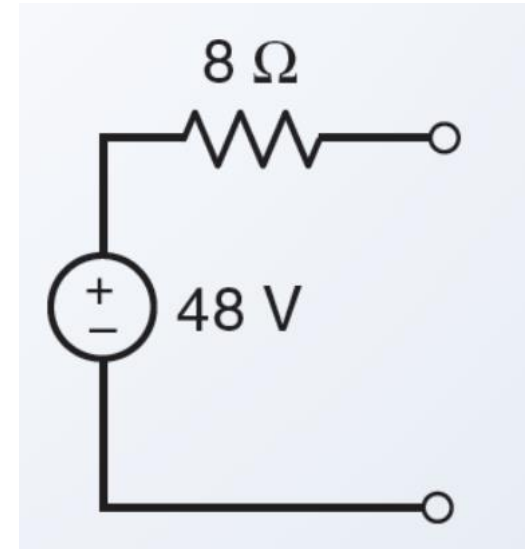


FIGURE 5.4-3 The Thévenin equivalent circuit involves three parameters: (a) the open-circuit voltage, v_{oc} , (b) the short-circuit current, i_{sc} , and (c) the Thévenin resistance, R_t .

The open-circuit voltage, v_{oc} , the short-circuit current, i_{sc} , and the Thévenin resistance, R_t , are related by the equation

$$v_{oc} = R_t i_{sc} \quad (5.4-2)$$



Example

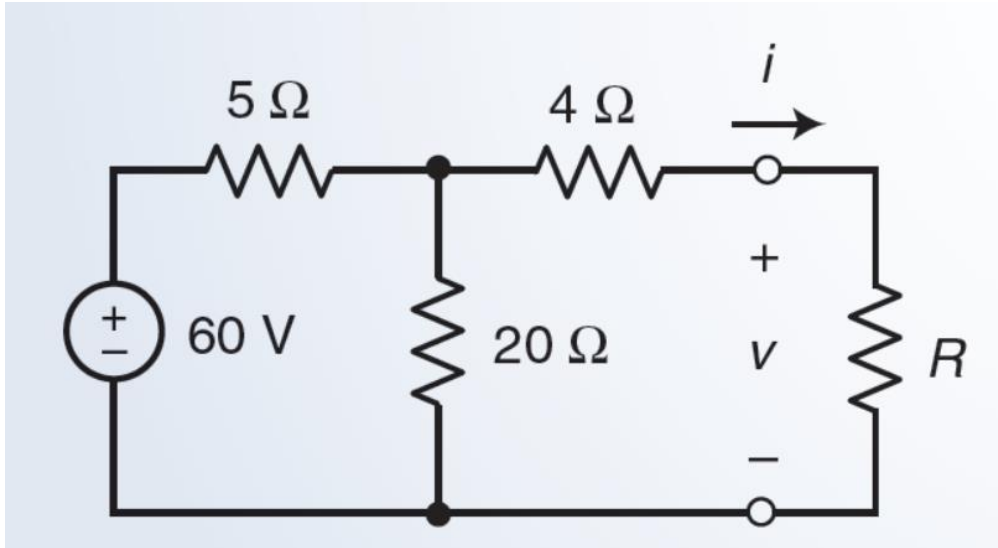

$$\frac{5 \times 20}{5 + 20} + 4 = 8 \Omega$$

$$60 \times \frac{20}{5 + 20} = 48 V$$


Example

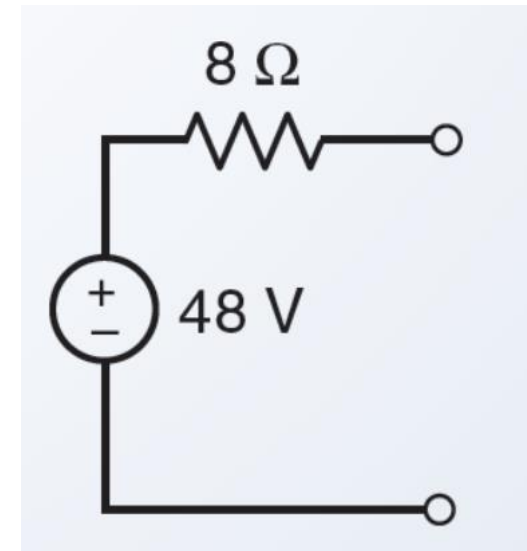
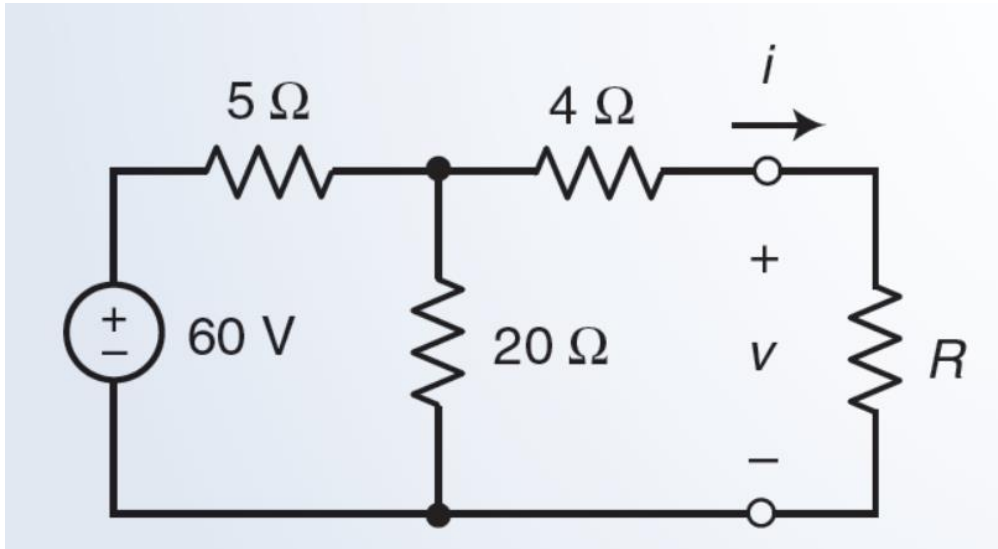



$$R = 0 \Rightarrow 5 + \frac{4 \times 20}{4 + 20} = 5 + \frac{10}{3} = \frac{25}{3} \Omega$$

$$i = \frac{60}{\left(\frac{25}{3}\right)} \times \frac{20}{4 + 20} = 6A \Rightarrow \frac{48}{6} = 8\Omega$$

Lab Circuit 2

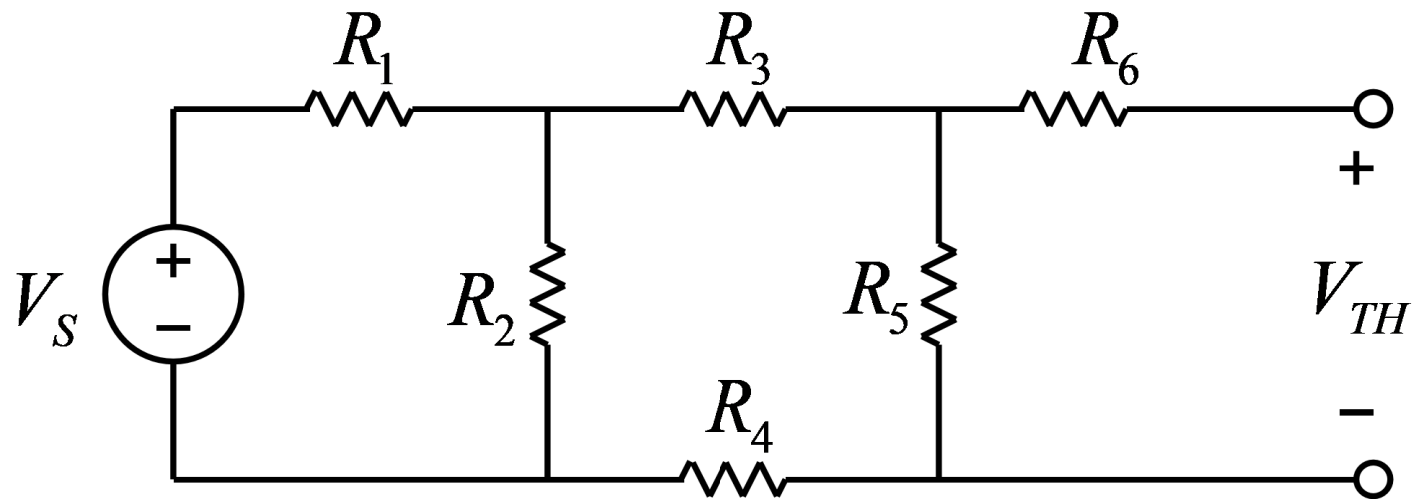

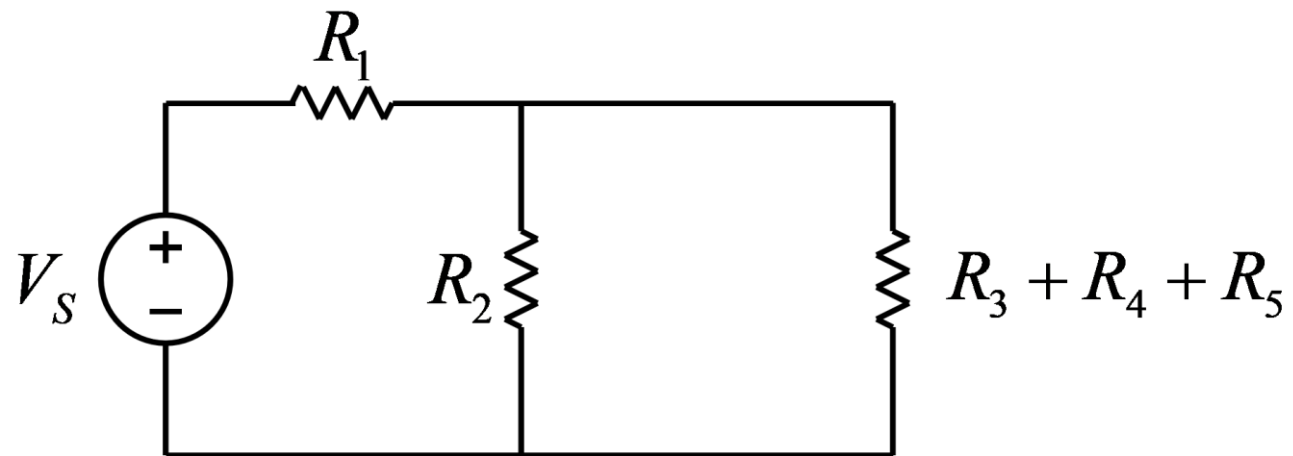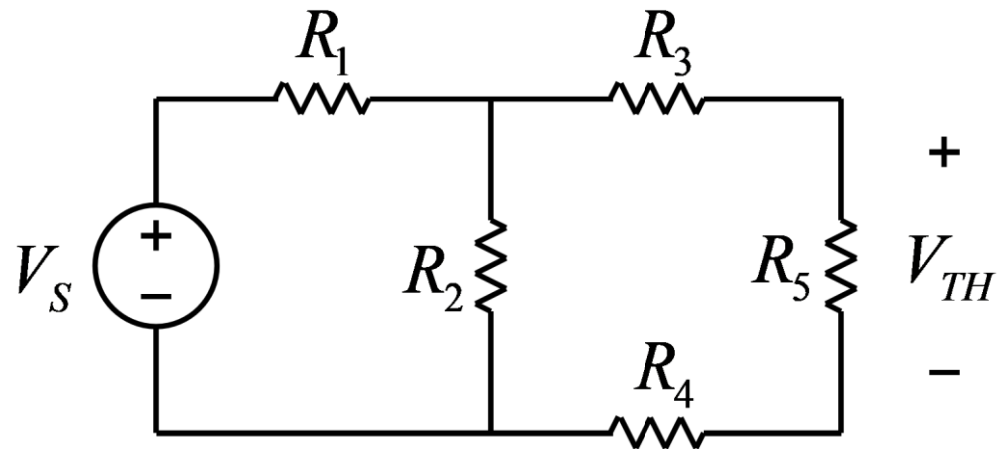

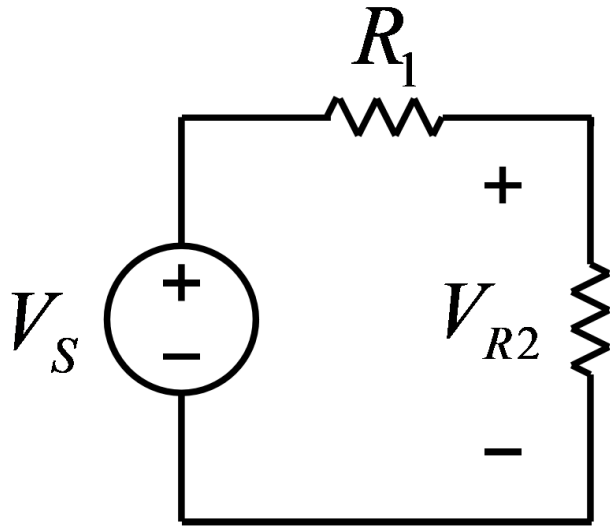



$$R_2 \parallel (R_3 + R_4 + R_5)$$

$$= \frac{R_2 (R_3 + R_4 + R_5)}{R_2 + (R_3 + R_4 + R_5)}$$

$$V_{R2} = V_S \frac{R_2 \parallel (R_3 + R_4 + R_5)}{R_1 + R_2 \parallel (R_3 + R_4 + R_5)}$$
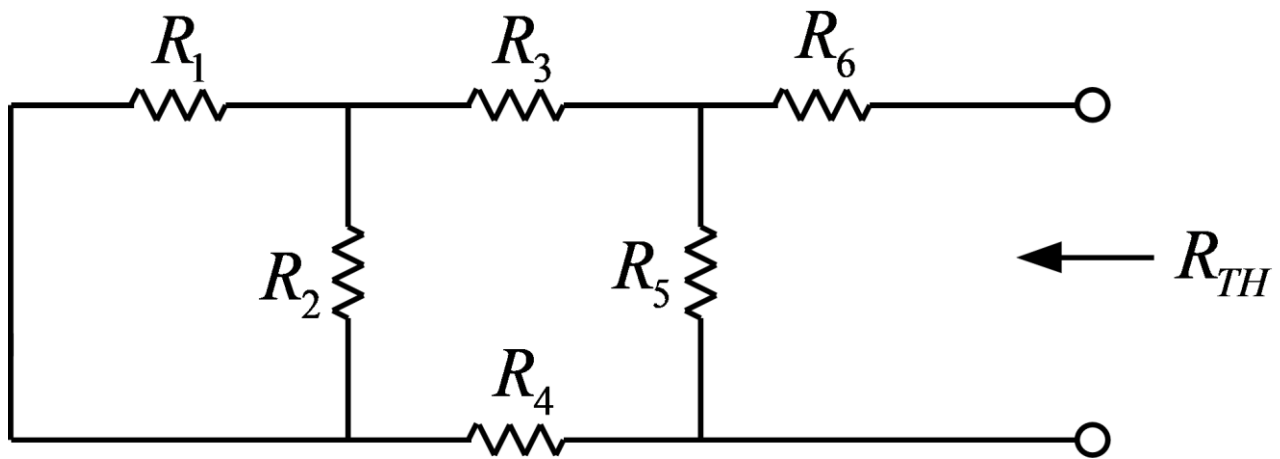
$$V_{TH} = V_{R2} \frac{R_5}{R_3 + R_4 + R_5}$$



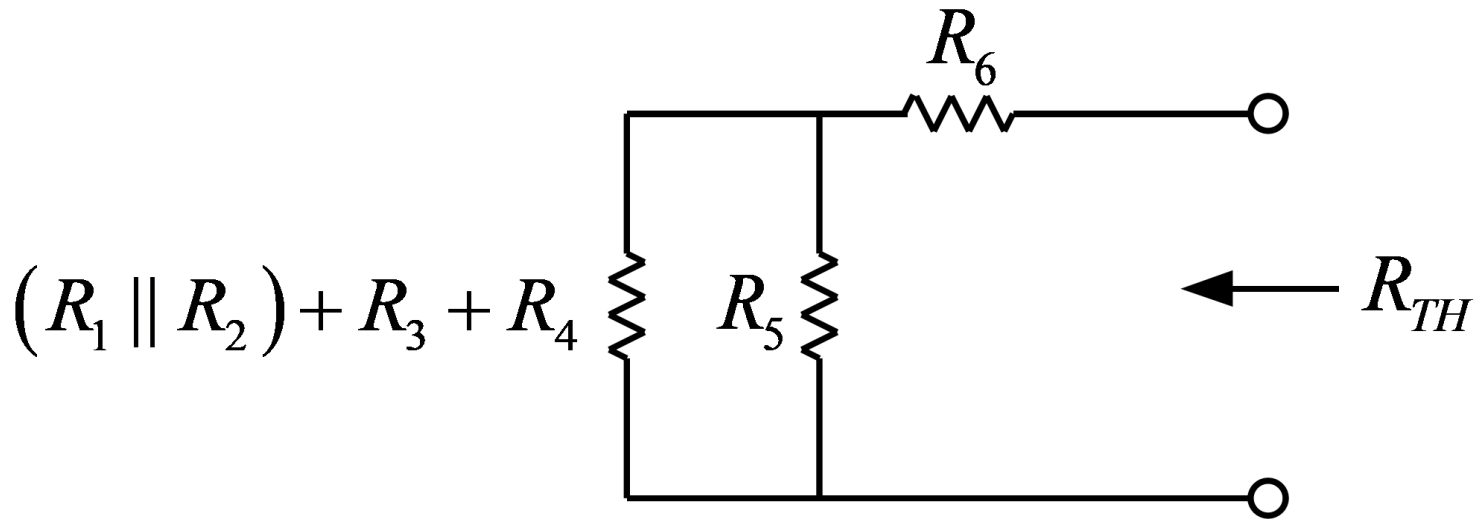

$$R_{TH} = \left(\left((R_1 \parallel R_2) + R_3 + R_4 \right) \parallel R_5 \right) + R_6$$